

⇒ Laplace Transformation -

$$\rightarrow t \rightarrow s = \sigma + j\omega.$$

Laplace Transformation,

$$F(s) = L[f(t)] = \int_0^{\infty} f(t) \cdot e^{-st} dt.$$

where s = frequency.

$$\begin{aligned} F(s) &= \int_0^{\infty} 1 \cdot e^{-st} dt \\ &= \frac{e^{-st}}{-s} \Big|_0^{\infty} \\ &= \frac{1}{s} \end{aligned}$$

⇒ Unit function -

$$u(t) = \begin{cases} 1, & t > 0 \\ 0, & t = 0 \end{cases}$$

$$f(t) = 1$$

$$\begin{aligned} F(s) &= \int_0^{\infty} f(t) \cdot e^{-st} dt \\ &= \int_0^{\infty} 1 \cdot e^{-st} dt \\ &= \frac{(e^{-st})}{-s} \Big|_0^{\infty} \\ &= -\frac{1}{s} [0 - 1] = \frac{1}{s}. \end{aligned}$$

\Rightarrow Ramp function -

$$f(t) = t$$

$$F(s) = ?$$

$$\begin{aligned} F(s) &= \int_0^\infty f(t) \cdot e^{-st} dt \\ &= \int_0^\infty t \cdot e^{-st} dt \\ &= \left(t \frac{e^{-st}}{-s} \right)_0^\infty - \frac{1}{-s} \int_0^\infty 1 \cdot e^{-st} dt \\ &= (0 - 0) + \frac{1}{s} \frac{(e^{-st})_0^\infty}{-s} \\ &= -\frac{1}{s^2} (0 - 1) \\ &= \frac{1}{s^2}. \end{aligned}$$

$$\Rightarrow f(t) = e^{-xt}.$$

$$F(s) = ?$$

$$\begin{aligned} F(s) &= \int_0^\infty f(t) \cdot e^{-st} dt \\ &= \int_0^\infty e^{-xt} \cdot e^{-st} dt \\ &= \int_0^\infty e^{-(x+s)t} dt. \\ &= \frac{1}{s+x} \end{aligned}$$

\Rightarrow 'sin' function -

$$\sin \omega t = \frac{e^{j\omega t} - e^{-j\omega t}}{2j}$$

$$f(t) = \sin \omega t.$$

$$F(s) = ?$$

$$\begin{aligned}
 F(s) &= \int_0^\infty f(t) \cdot e^{-st} dt \\
 &= \int_0^\infty \sin \omega t \cdot e^{-st} dt \\
 &= \int_0^\infty \left(\frac{e^{j\omega t} - e^{-j\omega t}}{2j} \right) e^{-st} dt \\
 &= \int_0^\infty \frac{e^{j\omega t} \cdot e^{-st}}{2j} dt - \int_0^\infty \frac{e^{-j\omega t} \cdot e^{-st}}{2j} dt \\
 &= \frac{1}{2j} \int_0^\infty e^{-t(-j\omega+s)} dt - \frac{1}{2j} \int_0^\infty e^{-t(j\omega+s)} dt \\
 &= \frac{1}{2j} \cdot \frac{1}{s-j\omega} - \frac{1}{2j} \cdot \frac{1}{s+j\omega} \\
 &= \frac{1}{2j} \left[\frac{1}{s-j\omega} - \frac{1}{s+j\omega} \right] \\
 &= \frac{1}{2j} \left[\frac{s+j\omega - s-j\omega}{s^2 - j\omega^2} \right] \\
 &= \frac{1}{2j} \left[\frac{2j\omega}{s^2 + \omega^2} \right] = \frac{\omega}{s^2 + \omega^2}.
 \end{aligned}$$

\Rightarrow find $L\{f'(t)\}$.

$$F(s) = \int_0^\infty f(t) \cdot e^{-st} dt.$$

$$F(s) = \left(F(t) - \frac{1}{s} e^{-st} \right)_0^\infty + \frac{1}{s} \int_0^\infty f'(t) e^{-st} dt$$

$$\therefore sF(s) = -f(t) \cdot e^{-st} + \int_0^\infty f'(t) \cdot e^{-st} dt$$

$$\therefore sF(s) = F(0^+) + L\{f'(t)\}.$$

$$\therefore sF(s) - F(0^+) = L\{f'(t)\}.$$

$$\Rightarrow \cos \omega t = \frac{1}{\omega} \frac{d}{dt} (\sin \omega t)$$

$$= \frac{1}{\omega} [sF(s) - F(0^+)]$$

$$= \frac{1}{\omega} \left[s - \frac{\omega}{s^2 + \omega^2} \right]$$

$$= \frac{s}{s^2 + \omega^2}$$

$$\Rightarrow L\{f(t)\} = \int_0^\infty f(t) \cdot e^{-st} dt.$$

$$\Rightarrow L\{Af_1(t) + Bf_2(t)\} = AF_1(s) + BF_2(s).$$

$$\Rightarrow L\left\{ \frac{d}{dt} f(t) \right\} = sF(s) - F(0^+).$$


$$\Rightarrow L\left\{ \int_{t_1}^{t_2} f(t) \cdot dt \right\} = \frac{1}{s} F(s).$$

⇒ Initial condition -

$$f(0^+) = \lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} s F(s).$$

⇒ Final condition -
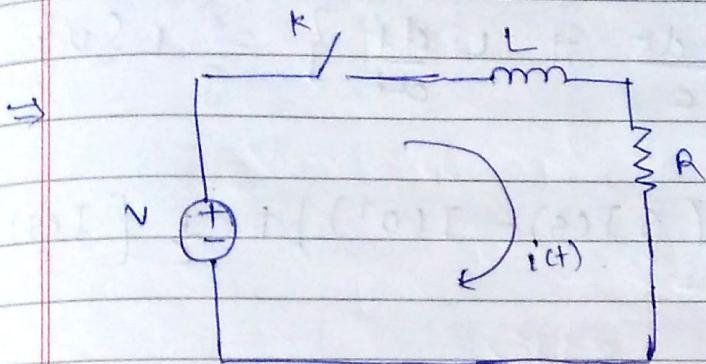
$$f(\infty) = \lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s).$$



$$\text{Here, } RI + L \frac{di}{dt} = V.$$


Now, we will take its Laplace,

$$L \left\{ RI + L \frac{di}{dt} \right\} = L\{V\}. = V L\{I\}.$$

$$\therefore R I(s) + L(sE(s) - f(0^+)) = V_s.$$

$$\therefore R I(s) + S L I(s) - L f(0^+) = V_s. \quad \text{initially zero.}$$
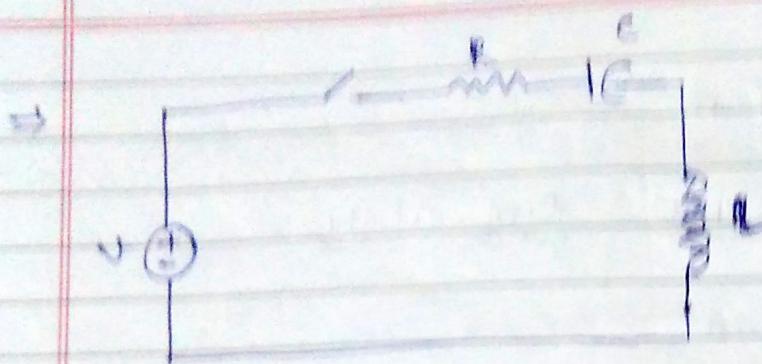
$$\boxed{\therefore I(s) = \frac{V_s}{R + sL}}$$



$$\text{Here, } RI + \frac{1}{C} \int i dt + L \frac{di}{dt} = V. \xrightarrow{\text{time domain}}$$

$$\therefore \{RI + \frac{1}{C} \int i dt + L \frac{di}{dt}\} = L\{V\}. \quad \xrightarrow{\text{initial}}$$

$$\rightarrow \therefore RI(s) + L(SI(s) - I(0^+)) + \frac{1}{C} [I(s) + 10] = \frac{V}{s}. \quad \xrightarrow{\text{initial}}$$

$$\therefore RI(s) + S I(s) + \frac{I(s)}{Cs} = \frac{V}{s}. \quad (1)$$

$$\therefore RCs I(s) + s^2 LC I(s) + I(s) = \frac{V}{s} \quad \xrightarrow{\text{Cs}}$$

$$\therefore I(s) [RCs + s^2 LC + 1] = \frac{V}{s}.$$

$$\therefore I(s) = \frac{\frac{V}{s}}{RCs + s^2 LC + 1}$$

$$\therefore I(s) = \frac{\frac{V}{s}}{R + LS + \frac{1}{Cs}}$$

⇒ Partial fractions -

$$\Rightarrow \frac{s-1}{s^2+3s+2} = \frac{s-1}{(s+2)(s+1)} = \frac{A}{s+2} + \frac{B}{s+1}$$

$$\therefore s-1 = A(s+1) + B(s+2).$$

$$\text{If } s = -2 \Rightarrow -3 = A(-2+1)$$

$$\therefore -3 = A(-1)$$

$$\therefore A = 3$$

partial)

$$\text{If } s = -1 \Rightarrow -2 = B(1)$$

$$\therefore B = -2.$$

$$\therefore \frac{s-1}{(s+2)(s+1)} = \frac{3}{s+2} + \frac{-2}{s+1}.$$

$$\Rightarrow \frac{1}{s[s^2+6s+9]} = \frac{1}{s[s^2+3s+3s+9]}$$

$$= \frac{1}{s[s(s+3)+3(s+3)]}$$

$$= \frac{1}{s[s+3]^2} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{(s+3)^2}$$

$$\therefore \frac{1}{s(s+3)^2} = \frac{A}{s} + \frac{B}{s+3} + \frac{C}{(s+3)^2}$$

$$\therefore 1 = A(s+3)^2 + B(s)(s+3) + C(s)$$

if $s = -3$

$$\therefore I = A(-3)$$

$$\therefore C = -\frac{1}{3}$$

if $s = 0$,

$$\therefore I = A(0)$$

$$\therefore A = \frac{1}{3}$$

if $s = -1$

$$\therefore I = A(1) + B(-2) + C(-1)$$

$$\therefore I = \frac{4}{9} - 2B + \frac{1}{3}$$

$$\therefore 2B = \frac{4}{9} + \frac{3}{9} - \frac{9}{9}$$

$$\therefore 2B = -\frac{2}{9}$$

$$\therefore B = -\frac{1}{9}$$

\Rightarrow Inverse Laplace -


$$L^{-1}[f(s)] = \frac{1}{2\pi j} \int_{\sigma-j\omega}^{\sigma+j\omega} f(s) \cdot e^{st} ds = f(t)$$

\Rightarrow find Laplace -

$$f(t) = \cos 4t + 2 \cdot e^{3t} + t + \frac{1}{2}t$$

$$\begin{aligned} L\{f(t)\} &= L\{\cos 4t\} + 2 \left[L\{e^{3t}\} \right] + L\{t\} \\ &\quad + \frac{1}{2} L\{t\}. \end{aligned}$$
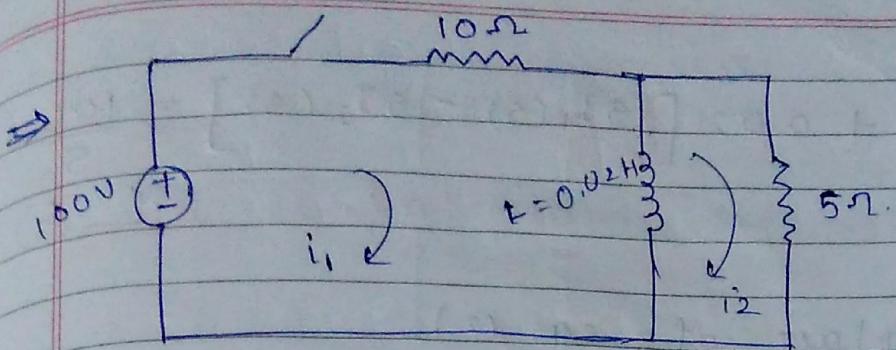
$$= \frac{1}{4} \cdot \frac{s}{s^2 + 16} + 2 \cdot \frac{1}{s+3} + \frac{1}{s^2} + \frac{1}{2} \cdot \frac{1}{s^2}$$



$$I = \frac{R \cdot L}{R + L} = \frac{5(0.02)}{5 + 0.02} =$$

$$\rightarrow 100 = R_i_1 + L \cdot \frac{di_1 - i_2}{dt}$$

$$\therefore 100 = 10i_1 + 0.02 \left(\frac{di_1}{dt} - \frac{di_2}{dt} \right) \quad \textcircled{1}$$

\rightarrow for loop - 2

~~$$\therefore 100 = R_1 i_1 + R_2 i_2$$~~

~~$$\therefore 100 = 10i_1 + 5i_2 \quad \textcircled{2}$$~~

$$0 = R_2 i_2 + L \frac{d(i_2 - i_1)}{dt}$$

$$\therefore 5i_2 + 0.02 \cdot \frac{d}{dt}(i_2 - i_1) = 0 \quad \textcircled{2}$$

\rightarrow Now, Laplace of eq. (1).

$$\therefore L \left\{ 10i_1 + 0.02 \left(\frac{di_1}{dt} - \frac{di_2}{dt} \right) \right\} = L \{ 100 \}$$

$$\therefore 10 \cdot I_1(s) + 0.02 \left[(sI_1(s) - I_1(0^+)) - (sI_2(s) - I_2(0^+)) \right] = 100 \cdot \frac{1}{s}$$

$$= 100 \cdot \frac{1}{s}$$

$$\therefore 10I_1(s) + 0.02 [sI_1(s) - sI_2(s)] = \frac{100}{s}$$

L(3)

and Laplace of eq. (2),

$$\therefore 10 \cdot 5 \cdot I_2(s) + 0.02 [(sI_2(s) - I_1(s)) - (sI_1(s) - I_2(s))] = 0$$

$$\therefore 5I_2(s) + 0.02 [sI_2(s) - sI_1(s)] = 0,$$

L(4)

from eq. (4),

$$sL(I_1(s) - I_2(s)) = \frac{100}{s} - 10I_1(s)$$

$$\therefore 5I_2(s) + sL[I_2(s) - I_1(s)] = 0,$$

$$\therefore 5I_2(s) + sL(I_2(s)) + sL I_1(s) = 0$$

$$\therefore (5 + sL) I_2(s) = -sL I_1(s)$$

$$\therefore I_2(s) = \frac{sL \cdot I_1(s)}{5 + sL} \quad \text{--- (5)}$$

put eq.(5) in eq.(3).

$$\therefore 10I_1(s) + 5L [I_1(s) - I_2(s)] = \frac{v}{s}.$$

$$\therefore 10I_1(s) + 5L [I_1(s) - \frac{5L \cdot I_1(s)}{5+5L}] = \frac{v}{s}.$$

$$\therefore 10I_1(s) + 5L \left[\frac{5I_1(s) + 5L \cdot I_1(s) - 5L \cdot I_1(s)}{5+5L} \right] = \frac{v}{s}.$$

$$\therefore 10I_1(s) + \frac{5SL}{5+5L} I_1(s) = \frac{v}{s}.$$


$$\therefore I_1(s) \left[10 + \frac{5SL}{5+5L} \right] = \frac{v}{s}.$$

$$\therefore I_1(s) \left[\frac{50 + 10SL + 5SL}{5+5L} \right] = \frac{v}{s}.$$

$$\therefore I_1(s) \left[\frac{50 + 15SL}{5+5L} \right] = \frac{v}{s}.$$

$$\therefore I_1(s) = \frac{v(5+5L)}{s(50+15SL)} \quad \text{--- (6)}$$

Ques

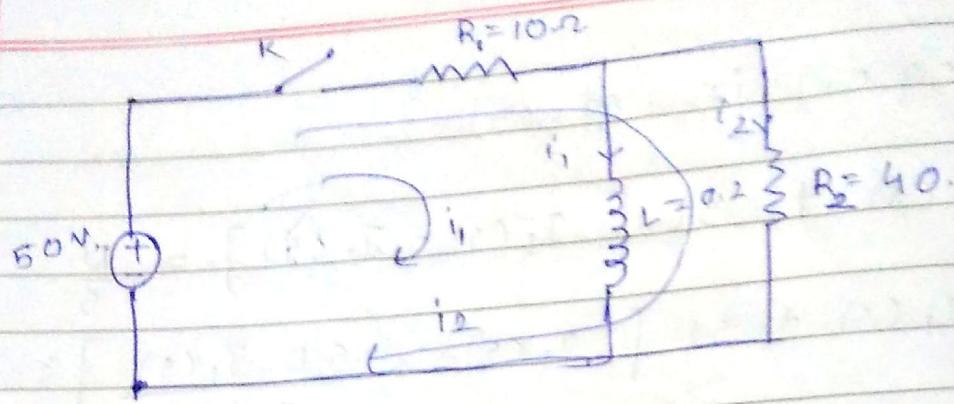

$$50 - 10i_1 + L \cdot \frac{di_1}{dt} = 0.$$

$$\therefore 50 = 10i_1 + L \cdot \frac{di_1}{dt} \quad \text{--- (1)}$$

→ for 2nd loop:

$$50 = 10(i_1 + i_2) + L \cdot \frac{di_2}{dt} \quad \text{--- (1)}$$

→ for 2nd loop,

$$50 = 10(i_1 + i_2) + 40i_2 \quad \text{--- (2)}$$

$$\therefore 50 = 10i_1 + 50i_2 \quad \text{--- (2)}$$

→ Laplace of 1st loop.

$$L\{50\} = L\{10(i_1 + i_2)\} + L\{0.2 \cdot \frac{di_1}{dt}\}$$

$$\therefore 50 \cdot \frac{1}{s} = 10 [I_1(s) + I_2(s)] + 0.2 \cdot [sI_1(s) - 1]$$

$$\therefore \frac{50}{s} = 10I_1(s) + 10I_2(s) + 0.2[sI_1(s) - 1]$$

$$\therefore \frac{50}{s} = (10 + LS)I_1(s) + 10I_2(s) - \frac{0.2}{s} \quad \text{--- (3)}$$

→ Laplace of 2nd loop -

$$L\{50\} = L\{10i_1\} + 50 \cdot L\{i_2\}$$

$$\therefore \frac{50}{s} = 10 \cdot I_1(s) + 50 I_2(s) \quad \text{--- (4)}$$

→ combining (3) and (4),

$$\begin{bmatrix} 10 & 40 \\ 10+LS & 10 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} 50/s \\ 50/s \end{bmatrix}$$

$$\therefore I_1(s) = \frac{\begin{vmatrix} 50 & 40 \\ 50/s & 10 \end{vmatrix}}{\begin{vmatrix} 10 & 40 \\ 10+LS & 10 \end{vmatrix}}$$

$$= \frac{|100 - 400|}{|100 - 400 - 40LS|}$$

$$\therefore I_1(s) = \frac{300}{300 + 40s}$$

$$\rightarrow \text{and } I_2(s) = \frac{\begin{vmatrix} 10 & 50/s \\ 10+LS & 50/s \end{vmatrix}}{\begin{vmatrix} 100 - 400 - 40LS \end{vmatrix}}$$

$$= \frac{\frac{500}{s} - \frac{500}{s}}{300 + 40s} - 50L$$

$$\therefore I_2(s) = \frac{50L}{300 + 40s}$$

$$(10 + LS)I_1(s) + 10I_2(s) = 10I_1(s) + 50I_2(s)$$

$$\cancel{10I_1(s)} + LS I_1(s) + 10I_2(s) = \cancel{10I_1(s)} + 10I_2(s)$$


$$\therefore LS I_1(s) - 40I_2(s) = 0.$$

$$\therefore I_1(s) = \frac{5}{s+0.625}, \quad I_2(s) = \frac{1}{s} - \frac{1}{s+0.625}$$

$$I^1(I_1(s)) = 5 \cdot e^{-0.625t}$$

$$I^1(I_2(s)) = 1 - e^{-0.625t}$$

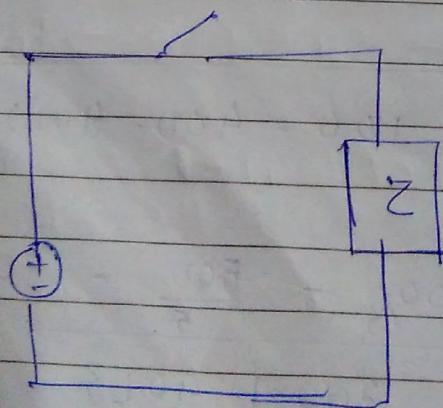\Rightarrow Obtain the equivalent impedance of the s domain network, find total current using current div. method. (same network as before)



$$Z = R_1 + \left(\frac{R_2 L}{R_2 + L} \right)$$

$$= 10 + \left(\frac{40 \times 0.2}{40.2} \right)$$

$$Z = R_1 + \left(\frac{R_2 \cdot \omega_L}{R_2 + \omega_L} \right)$$

$$= 10 + \frac{\left(\frac{40}{0.2\$} \right)}{\left(40 + \frac{1}{0.2\$} \right)} = 10 + \left(\frac{40 \times 0.2\$}{40 + 0.2\$} \right)$$

$$= 10 + \frac{\frac{200}{\$}}{\frac{8\$ + 1}{0.2\$}} = \frac{400 + 2\$ + 8\$}{40 + 0.2\$}$$

$$= 10 + \frac{40}{8\$ + 1} = \frac{400 + 10\$}{40 + 0.2\$}$$

$$= \frac{80\$ + 10 + 40}{8\$ + 1}$$


$$= \frac{80\$ + 50}{8\$ + 1}$$

$$\therefore I = \frac{50/\$}{Z}$$

$$= \frac{50/\$ (40 + 0.2\$)}{400 + 10\$}$$

$$\therefore I = \frac{50 (40 + 0.2\$)}{5 (400 + 10\$)} = I_1 + I_2,$$

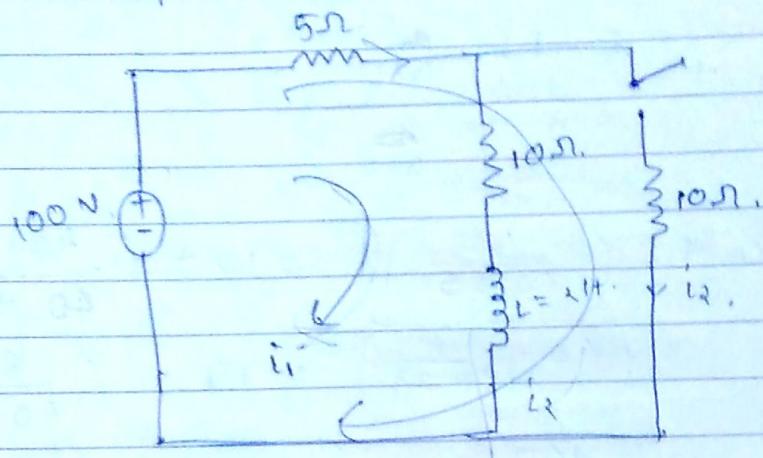A 100V source passing a continuously
At time $t=0$, switch is closed with
 10Ω parallel resistor. find the
Laplace of resultant current.



$$\text{Hence } I(0^+) = \frac{100}{5+10} = \frac{100}{15} = 20\% \text{ A.} = I(0^+)$$

→ for first loop,

$$100 - 5(i_1 + i_2) = 10i_1 - \frac{1}{\epsilon} \frac{di_1}{dt}$$

$$\therefore 100 = 15i_1 + 5i_2 + L \frac{di_1}{dt} \quad \leftarrow (1)$$

→ for second loop.

$$100 - 5(i_1 + i_2) - 10i_3 = 0.$$

$$\therefore 100 = 15i_1 + 15i_2 \quad - \textcircled{2}$$

→ taking laplace of eq. (1).

$$\mathcal{L}\{100\} = 15 \mathcal{L}\{i_1\} + 5 \mathcal{L}\{i_2\} + 2 \mathcal{L}\left\{\frac{di_1}{dt}\right\}$$

$$\therefore \frac{100}{\$} = 15 I_1(s) + 5 I_2(s) + 2(5 I_1(s) - I_2(s))$$

$$\therefore \frac{100}{\$} = 15 I_1(s) + 5 I_2(s) + 25 I_1(s) - 2\left(\frac{20}{3}\right)$$

$$\therefore \frac{100}{\$} = (15 + 25) I_1(s) + 5 I_2(s) - \frac{40}{3}$$

$$\therefore \frac{100}{\$} + \frac{40}{3} = (15 + 25) I_1(s) + 5 I_2(s) \quad \boxed{③}$$

→ taking laplace of eq. (2),

$$\mathcal{L}\{100\} = 5 \mathcal{L}\{i_1\} + 15 \mathcal{L}\{i_2\}$$

$$\therefore \frac{100}{\$} = 5 I_1(s) + 15 I_2(s) \quad \text{--- (4)}$$

~~$$\therefore \frac{300}{\$} = 15 I_1(s) + 75 I_2(s)$$~~

~~$$\frac{100}{\$} + \frac{40}{3} = 15 I_1(s) + 25 I_1(s) + 5 I_2(s)$$~~

~~$$\frac{300}{\$} = 15 I_1(s) + 75 I_2(s)$$~~

~~$$\frac{40}{3} - \frac{200}{\$}$$~~

→ Multiplying eq.(8) by 5,

$$\therefore \frac{300}{\$} + 40 = (70 + 6\$) I_1(s) + 15 I_2(s)$$
$$\frac{100}{\$} = 5 I_1(s) + 15 I_2(s)$$

$$\frac{200}{\$} + 40 = (70 + 6\$) I_1(s).$$

$$\therefore I_1(s) = \frac{\frac{200}{\$} + 40}{70 + 6\$}$$

$$\boxed{\therefore I_1(s) = \frac{200 + 40\$}{\$ (70 + 6\$)}} \quad \text{--- A}$$

and, $\frac{100}{\$} = \left[\frac{200 + 40\$}{\$ (70 + 6\$)} \right] 5 + 15 I_2(s)$

(\because from eq.(9))

$$\therefore \frac{20}{\$} = \frac{200 + 40\$}{\$ (70 + 6\$)} + 3 I_2(s).$$

$$\therefore \frac{20}{\$} - \frac{200 + 40\$}{\$ (70 + 6\$)} = 3 I_2(s)$$

$$\therefore \frac{400 + 120\$ - 200 - 40\$}{\$ (70 + 6\$)} = 3 I_2(s).$$

$$\therefore \frac{1200 + 80\$}{\$ (70 + 6\$)} = 3 I_2(s).$$

$$\boxed{I_2(s) = \frac{1}{3\$} \left[\frac{1200 + 80\$}{70 + 6\$} \right]}$$


$$\frac{200 + 40\$}{\$ (70 + 6\$)} = \frac{A}{\$} + \frac{B}{70 + 6\$}$$

$$\therefore 200 + 40\$ = A(70 + 6\$) + B\$.$$

$$\rightarrow B = 0, \quad \Rightarrow \quad 200 = A(70) \\ \therefore A = 200/70$$


Ques-

(i) initial value of current.

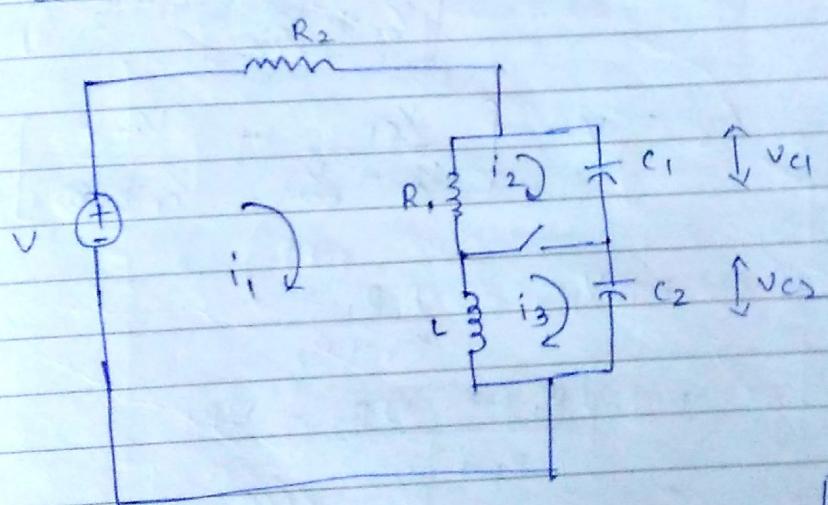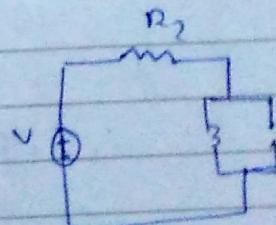(ii) at $t=0^-$ current.(iii) at $t=0$ what are the various currents.

$$\text{at } t=0^-, \quad i_{R_1}(0^-) = \frac{V}{R_1 + R_2}$$

$$\therefore i_{R_1}(0^-) = i_L(0^-) = \frac{V}{R_1 + R_2}$$



$$\text{At } q_1 = q_2$$

$$\therefore C_1 V_{C1} = C_2 V_{C2}$$

$$\therefore \frac{V_{C1}}{V_{C2}} = \frac{C_2}{C_1}$$

$$\text{and } V_{C1} = \frac{Y_{C1}}{\frac{1}{C_1} + \frac{1}{C_2}} \left(\frac{V}{R_1 + R_2} \right) (R_1)$$

$$\text{and } V_{C2} = \frac{Y_{C2}}{\frac{1}{C_1} + \frac{1}{C_2}} \left(\frac{V}{R_1 + R_2} \right) (R_2)$$

$$\rightarrow \text{at } t=0^+$$

$$V - i_1 R_2 - V_{C1} - V_{C2} = 0$$

$$\therefore i_1 R_2 = V - V_{C1} - V_{C2}$$

$$\therefore i_1 R_2 = V - \left[\frac{Y_{C1}}{Y_{C1} + Y_{C2}} \left(\frac{V \cdot R_1}{R_1 + R_2} \right) \right] - \left[\frac{Y_{C2}}{Y_{C1} + Y_{C2}} \left(\frac{V \cdot R_2}{R_1 + R_2} \right) \right]$$

$$= V - \left[\frac{Y_{C1}}{Y_{C1} + Y_{C2}} + \frac{Y_{C2}}{Y_{C1} + Y_{C2}} \right] \frac{VR_1}{R_1 + R_2}$$

$$= V - \frac{VR_1}{R_1 + R_2}$$

$$= \frac{VR_1 + VR_2 - VR_1}{R_1 + R_2}$$

$$\therefore i_1 R_2 = \frac{VR_2}{R_1 + R_2}$$

$$\therefore i_1 = \frac{V}{R_1 + R_2}$$

$$\bullet \quad V_{C_1} + R_1(i_2 - i_1)$$

$$i_1(0^+) = i_1(0^+) - i_3(0^+)$$

$$\therefore \frac{V}{R_1 + R_2} = \frac{V}{R_1 + R_2} - i_3(0^+)$$

$$\rightarrow \text{at } t=0^+, \quad i_3(0^+) = 0.$$

$$\therefore R_1 [i_1(0^+) - i_2(0^+)] = V_{C_1}.$$

$$\therefore R_1 \left(\frac{V}{R_1 + R_2} - i_2 \right) = \frac{\gamma_{C_1}}{\gamma_{C_1} + \gamma_{C_2}} \left(\frac{VR_1}{R_1 + R_2} \right)$$


$$\therefore \frac{VR_1}{R_1 + R_2} - i_2 R_1 = \frac{\gamma_{C_1}}{\gamma_{C_1} + \gamma_{C_2}} \left(\frac{VR_1}{R_1 + R_2} \right)$$

$$\therefore \left[1 - \frac{\gamma_{C_1}}{\gamma_{C_1} + \gamma_{C_2}} \right] \frac{VR_1}{R_1 + R_2} = i_2 R_1$$

$$\therefore \left[\frac{\gamma_{C_1} + \gamma_{C_2} - \gamma_{C_1}}{\gamma_{C_1} + \gamma_{C_2}} \right] \frac{VR_1}{R_1 + R_2} = i_2 R_1$$

$$\therefore i_2 = \left(\frac{\frac{1}{C_2}}{\gamma_{C_1} + \gamma_{C_2}} \right) \frac{V}{R_1 + R_2}$$

Ques.

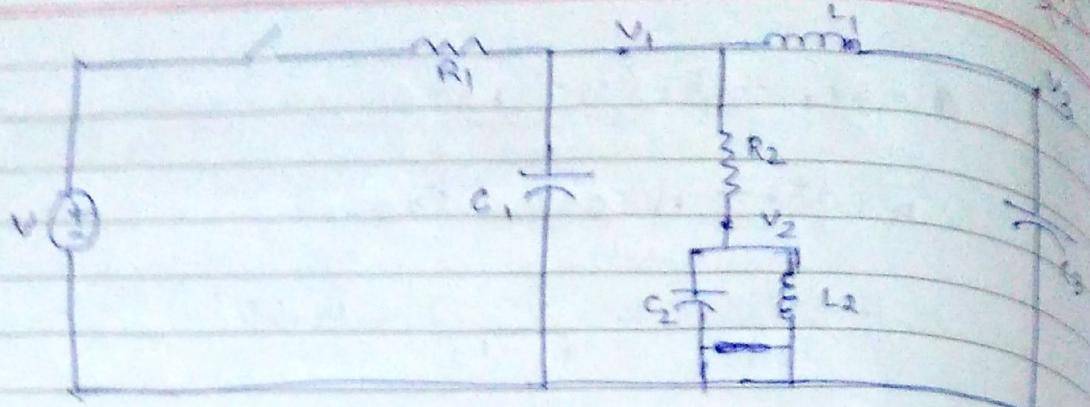


$$\rightarrow \frac{v_1 - V}{R_1} + \frac{v_1 - v_2}{R_2} + C_1 \cdot \frac{dv_1}{dt} + \frac{1}{L_1} \int (v_1 - v_2) dt = 0.$$


$$\rightarrow \frac{v_2 - v_1}{R_2} + C_2 \cdot \frac{dv_2}{dt} + \frac{1}{L_2} \int v_2 \cdot dt = 0.$$

$$\rightarrow C_3 \cdot \frac{dv_3}{dt} + \frac{1}{L_1} \int (v_3 - v_1) \cdot dt = 0.$$

Ques.

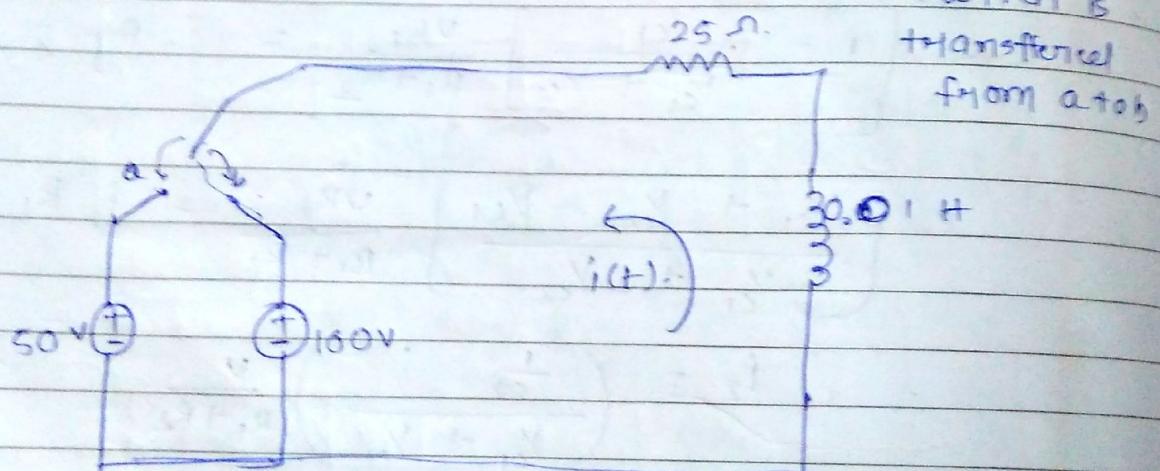

\rightarrow at $t = 0^+$,

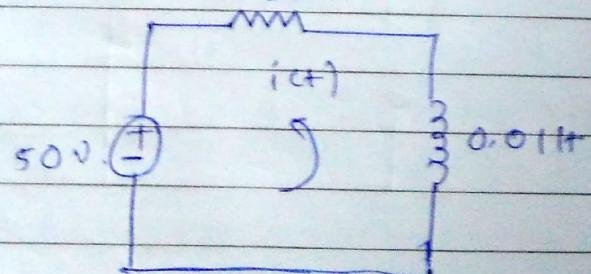

$$I(0^+) = -2 \text{ A}$$

KVL for loop, for $\underline{I(0^+)}$,

$$-\frac{100}{s} - L \cdot \frac{di}{dt} - 25i = 0,$$

$$\therefore -\frac{100}{s} = 0.01 \frac{di}{dt} - 25i$$

$$\therefore L \left\{ -\frac{100}{s} \right\} = 0.01 L \left\{ \frac{di}{dt} \right\} + 25 \cdot L \{ i \} =$$

$$\therefore -\frac{100}{s} / s = 0.01 [5I(s) - I(0^+)] + 25 I(s).$$

$$\therefore -\frac{100}{s^2} = 0.01 s I(s) + 25 I(s) - 0.01 I(0^+)$$

$$\therefore -\frac{100}{s^2} = [25 + 0.01s] I(s) - 0.01 \times 2.$$

$$(\because I(0^+) = \frac{50}{0.05} = 2A)$$

due to opposite

$$\therefore -\frac{50/s + 0.02}{25 + 0.01s} = I(s)$$

$$\therefore -\frac{50 + 0.02s}{s(25 + 0.01s)} - \frac{0.02}{25 + 0.01s} = I(s)$$

$$\frac{-50}{s(25 + 0.01s)} = \frac{A}{s} + \frac{B}{25 + 0.01s}$$

$$\therefore -50 = A(25 + 0.01s) + Bs$$

$$\Rightarrow s=0 \Rightarrow -50 = A(25)$$


$$\therefore A = -2$$

$$\Rightarrow s = -2500 \Rightarrow -50 = B(-2500)$$


$$\therefore B = 0.02$$

and so, $\frac{-2}{s} = I(s)$
 $\therefore i(\phi) = -2 A.$

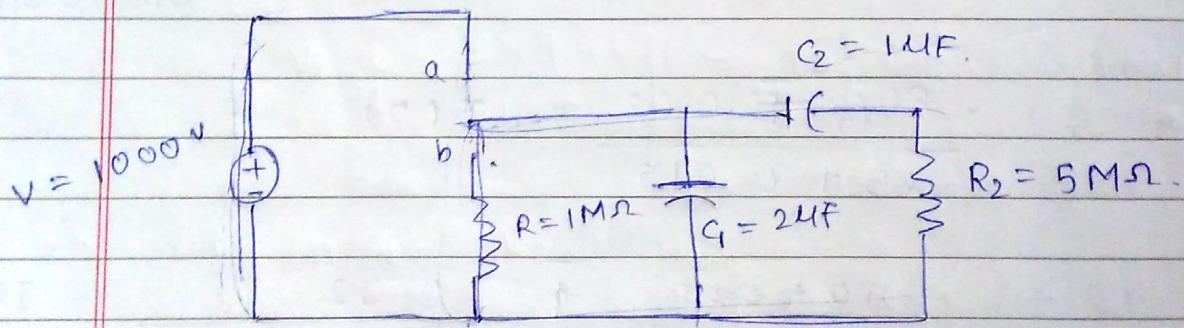Ques. steady state analysis at when connected to
~~at $t=0$~~ a at time $t=0$.




→ at $t = 0^+$:

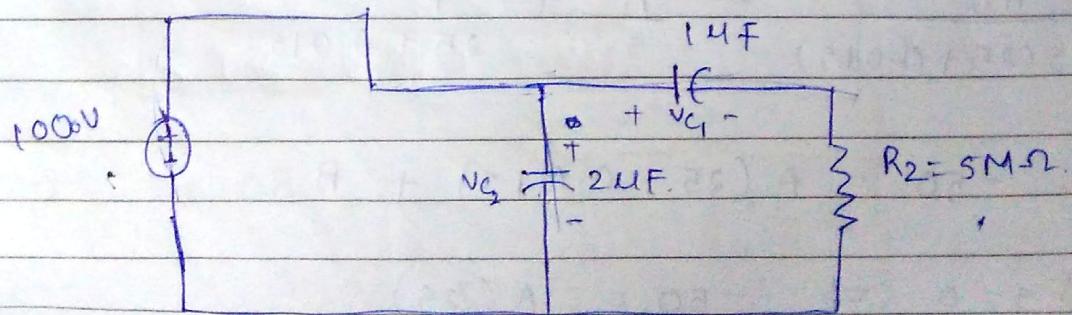


$$V_{C1} = V_{C2} = V \quad \text{at } t=0^+$$

so. Open circuit current $I(t=0^+) = 0$.

At $t=0^+$,

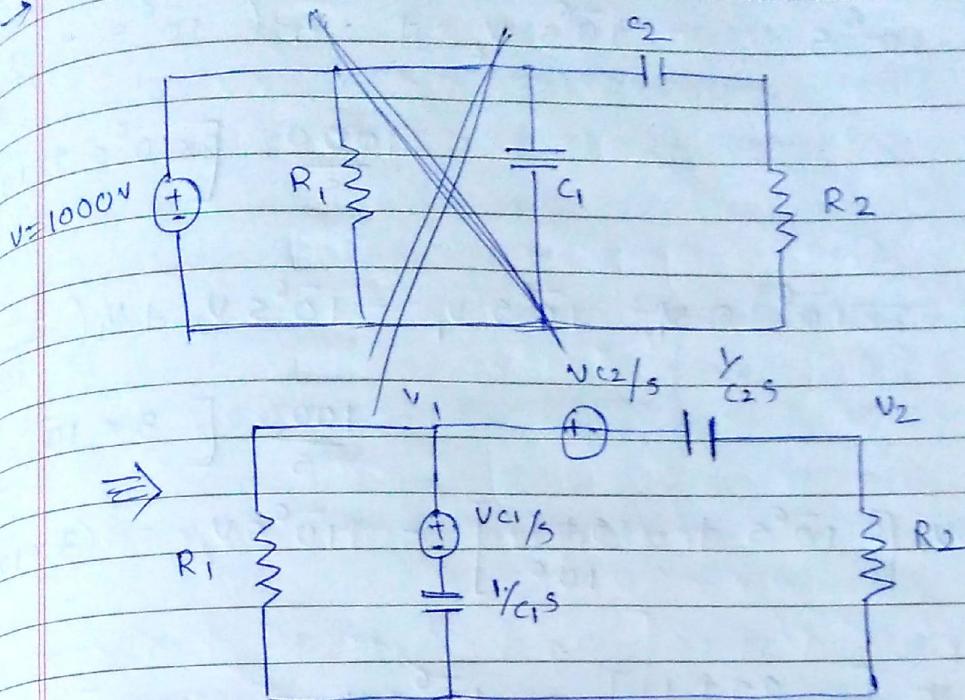

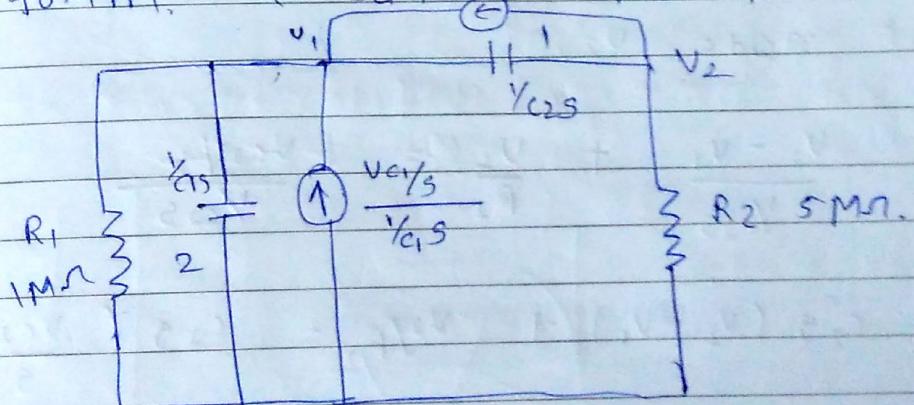Now, convert voltage source in current form. (current transformation)



Now, nodal circuit.

$$\frac{V_1 - V_2}{Y_{C2S}} + \frac{V_1}{R_1} + \frac{V_1}{Y_{C1S}} = \frac{V_{C1}/s}{Y_{C1S}} + \frac{V_{C2}/s}{Y_{C2S}}$$

$$\therefore V_2 s V_1 - C_2 s V_2 + V_1 \left(\frac{1}{R_1} + C_1 s \right)$$

$$= \frac{1000}{s} [C_1 s + C_2 s]$$

$$\therefore 10^6 s V_1 - 10^6 s V_2 + V_1 \left(10^6 s + \frac{1}{10^6} \right)$$

$$= \frac{1000}{s} [2 \times 10^6 s + 10^6 s]$$

$$\therefore (2 \times 10^6) s V_1 - 10^6 s V_1 - 10^6 s V_2 + V_1 \left(\frac{s+1}{10^6} \right)$$

$$= \frac{1000}{s} [3 \times 10^6 s],$$

$$\therefore V_1 \left[10^6 s + \frac{s+1}{10^6} \right] - 10^6 s V_2 = (3 \times 10^6) \frac{1000}{s}$$

$$\therefore V_1 \left[\frac{2s+1}{10^6} \right] - 10^6 s V_2 = \frac{3000 \times 10^6}{s} \quad \text{--- (1)}$$

→ At node V_2 ,

$$\frac{V_2 - V_1}{C_2 s} + \frac{V_2}{R_2} = \frac{V_{C_2}/s}{C_2 s}$$

$$\therefore C_2 s (V_2 - V_1) + V_2 / R_2 = C_2 s \left(\frac{V_{C_2}}{s} \right)$$

A

Fourier Series

classmate

Date _____
Page _____


If any signal,

$$\text{ex. } y(t) = \int e^{st} f(t) dt = e^{st} \int f(t) e^{-st} dt$$


↓

eigen-function
eigen value

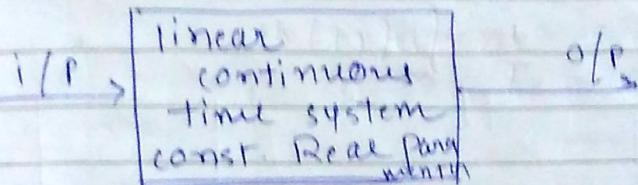Signal should not be changed with respect to time.


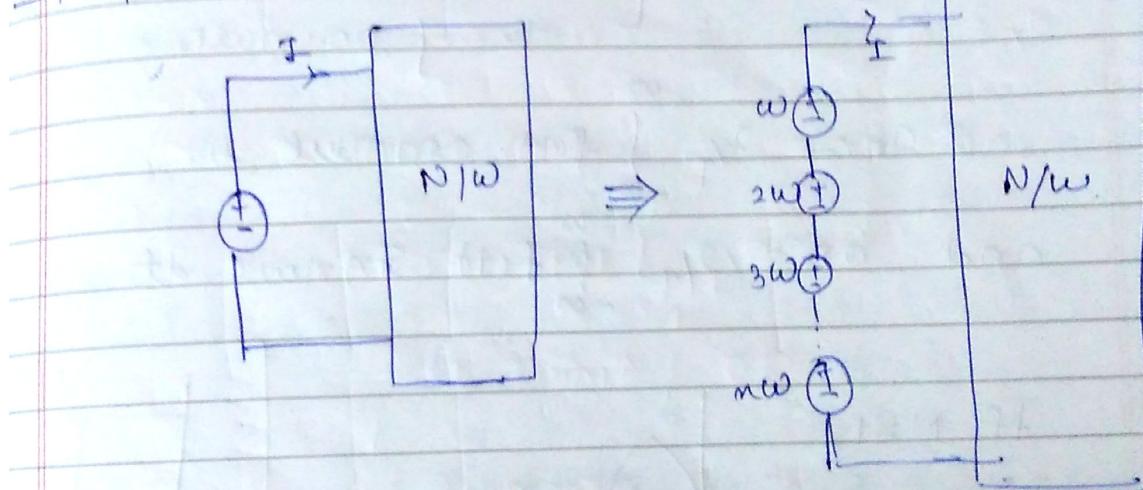
$$f(t) = a_0 + \sum a_n \cos n\omega t + b_n \sin n\omega t$$



$$\rightarrow f(t) = f(t + T_0), \quad T_0 = \text{Periodic time}$$

$f = \frac{1}{T_0}$ (frequency)

$\omega = \text{Angular frequency}$.

$$f(t) = a_0 + a_1 \cos \omega t + a_2 \cos 2\omega t + \dots + a_n \sin n\omega t + a_{n+1} \sin (n+1)\omega t + \dots$$

$$\therefore \int_{-\infty}^{\infty} f(t) dt = \int_{-\infty}^{\infty} [a_0 + a_1 \cos \omega t + a_2 \cos 2\omega t + \dots] dt$$

but Summation of Sinusoidal Signal will be zero.

$$\therefore \int_{-\infty}^{\infty} f(t) dt = a_0 T.$$

$$\therefore a_0 = \frac{1}{T} \int_{-\infty}^{\infty} f(t) dt.$$



Now, if we multiply with $\cos n\omega t$ then,

$$\cos n\omega t \cdot f(t) = [a_0 + a_1 \cos \omega t + a_2 \cos 2\omega t + \dots] \cos n\omega t.$$


$$\therefore a_n = \frac{2}{T} \int_{-\infty}^{\infty} f(t) \cdot \cos n\omega t dt.$$


$$\text{and } b_n = \frac{2}{T} \int_{-\infty}^{\infty} f(t) \cdot \sin n\omega t dt.$$

If $N=1$,

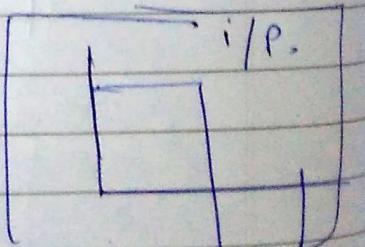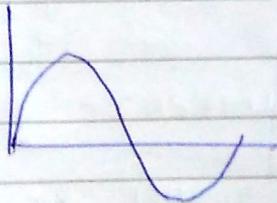


$N=2$

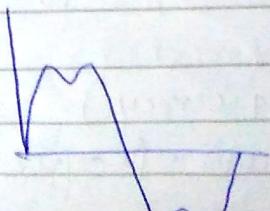

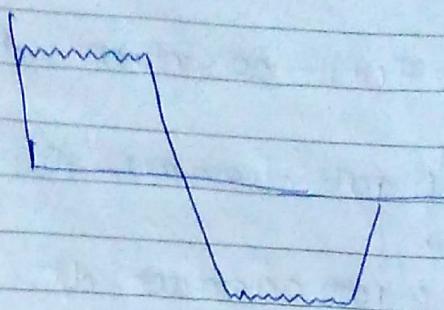$N=49$ 

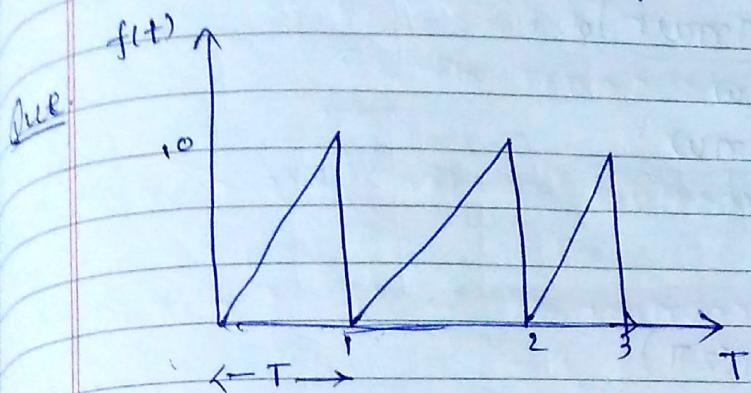so. at the receiving end, we can get almost same signal.



find $a_0, a_n b_n = ?$

$$f(t) = mx + c$$

here, $m = 10$ (\because slope)

$$\therefore f(t) = 10t$$

$$\therefore f(t) = a_0 + \sum_{n=1}^{\infty} [a_n \cos n\omega t + b_n \sin n\omega t]$$

$$\therefore 10t = a_0 +$$

$$\therefore a_0 = \frac{1}{T} \int_0^T f(t) \cdot dt$$

$$= \frac{1}{T} \int_0^T 10t \cdot dt$$

$$\therefore a_0 = 10.$$

$$\therefore a_0 = \int_0^T 10t \cdot dt = \frac{10 \cdot (t^2)}{2} = 5(1-0) = 5$$

$$\therefore a_0 = 5$$

$$a_n = \frac{2}{T} \int_0^T f(t) \cdot \cos n\omega t \cdot dt.$$

$$= \frac{2}{T} \int_0^T 10t \cos n\omega t \cdot dt.$$

$$= \frac{2}{T} \int_0^1 10t \cos n\omega t \cdot dt.$$

$$= \cancel{\frac{2}{T}} \frac{20}{\pi} \int_0^1 t \cos n\omega t \cdot dt.$$

$$= 20 \left(\frac{\sin n\omega t}{n\omega} \right)_0^1$$

$$= \frac{20}{n\omega} \sin n\omega$$

$$(n\omega = 2\pi)$$

$$= \frac{20}{n(2\pi)} \sin n(2\pi)$$

$$\therefore a_n = 0,$$

and $b_n = \frac{2}{T} \int_0^T f(t) \cdot \sin n\omega t \cdot dt.$

$$= \frac{2}{T} \int_0^1 10t \sin n\omega t \cdot dt.$$

$$= 20 \int_0^1 \sin n\omega t \cdot dt$$


$$= 20 \left(\frac{-\cos n\omega t}{n\omega} \right)_0^1$$

$$= \frac{20}{n\omega} (-\cos n\omega + 1)$$

$$= \frac{20}{n(2\pi)} (-\cos n(2\pi) + 1)$$

$$= \frac{20}{n(2\pi)}$$

$$\begin{aligned}
 &= \frac{20}{T} \int_0^T t \cdot \sin n\omega t \cdot dt \\
 &= 20 \int_0^T t \cdot \sin n\omega t \cdot dt \\
 &= 20 \left[\left(t \cdot \int \sin n\omega t \cdot dt \right)' - \int \left(\int \sin n\omega t \cdot dt \right) dt \right] \\
 &= 20 \left[\left(t \left(-\frac{\cos n\omega t}{n\omega} \right) \right)' - \int -\cos n\omega t \cdot dt \right] \\
 &= 20 \left[-\frac{1}{n\omega} + \int \cos n\omega t \cdot dt \right] \\
 &= 20 \left[-\frac{1}{n\omega} + \frac{(\sin n\omega t)'}{n\omega} \right] \\
 &= 20 \left[-\frac{1}{n\omega} + 0 \right] \\
 &= -\frac{20}{n(2\pi)} \\
 &= -\frac{10}{n\pi}
 \end{aligned}$$

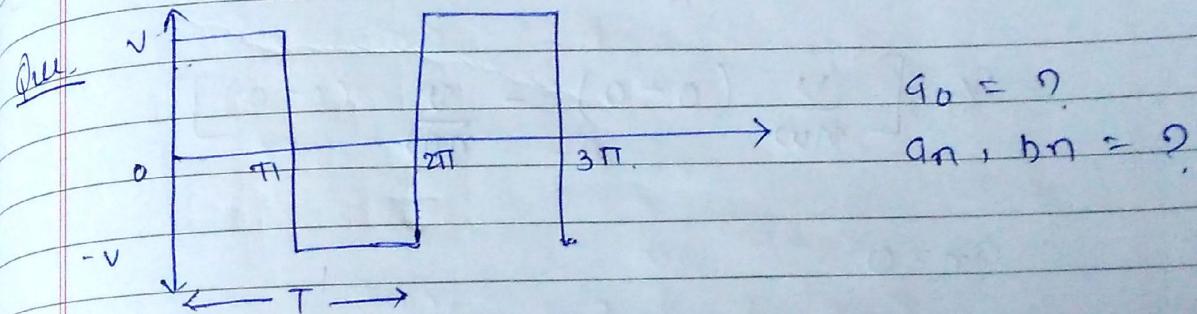

Here, $f(t) = \begin{cases} v, & 0 < \omega t < \pi, \\ -v, & \pi < \omega t < 2\pi. \end{cases}$

$$\begin{aligned}
 a_0 &= \frac{1}{T} \int_0^T f(t) \cdot dt \\
 &= \frac{1}{\pi} \left[\int_0^\pi f(t) \cdot dt + \int_\pi^{2\pi} f(t) \cdot dt \right]
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{1}{2\pi} \left[\int_0^\pi u \cdot dt + \int_\pi^{2\pi} -v \cdot dt \right] \\
 &= \frac{1}{2\pi} \left[v(t) \Big|_0^\pi - u(t) \Big|_\pi^{2\pi} \right] \\
 &= \frac{1}{2\pi} [v(\pi) - v(0)]
 \end{aligned}$$

$$\therefore a_0 = 0.$$

$$\begin{aligned}
 \rightarrow a_n &= \frac{2}{T} \int_0^T f(t) \cdot \cos n\omega t \cdot dt \\
 &= \frac{2}{T} \left[\int_0^\pi u \cdot \cos n\omega t \cdot dt + \int_\pi^{2\pi} -v \cdot \cos n\omega t \cdot dt \right] \\
 &= \frac{2}{T} \left[v \int_0^\pi \cos n\omega t \cdot dt - v \int_\pi^{2\pi} \cos n\omega t \cdot dt \right] \\
 &= \frac{2}{T} \left[v \frac{(\sin n\omega t)_0}{n\omega} - v \frac{(\sin n\omega t)_\pi}{n\omega} \right] \\
 &= \frac{2}{T} \left[\frac{v}{n\omega} (0-0) - \frac{v}{n\omega} (0-0) \right]
 \end{aligned}$$

$$\therefore a_n = 0$$

$$\begin{aligned}
 b_n &= \frac{2}{T} \int_0^T f(t) \sin n\omega t \, dt \\
 &= \frac{2}{T} \left[\int_0^{\pi} v \cdot \sin n\omega t \, dt + \int_{\pi}^{2\pi} (-v) \cdot \sin n\omega t \, dt \right] \\
 &= \frac{2}{T} \left[v \int_0^{\pi} \sin n\omega t \, dt - v \int_{\pi}^{2\pi} \sin n\omega t \, dt \right] \\
 &= \frac{2}{T} \left[v \cdot \frac{(-\cos n\omega t)}{n\omega} \Big|_0^{\pi} + v \cdot \frac{(\cos n\omega t)}{n\omega} \Big|_{\pi}^{2\pi} \right] \\
 &= \frac{2}{T} \left[-v \left(\frac{-\cos n\pi\omega}{n\omega} + 1 \right) + v \left(\frac{1 - \cos n\pi\omega}{n\omega} \right) \right] \\
 &= \frac{2v}{n\omega} \left[-\cos n\pi\omega + 1 - \cos n\pi\omega \right] \\
 &= \frac{2v(2\pi)}{n(2\pi)} \left[-2 \cos n\pi\omega \right] \\
 &= \frac{2v}{n} \left[-2 \cos n\pi\omega \right].
 \end{aligned}$$

$$\begin{aligned}
 &= \frac{dv}{nT} \left[- \left[\frac{w\sin t}{n} \right]_0^{\pi} + \left[\frac{w\sin t}{n} \right]_{\pi}^{2\pi} \right] \\
 &\approx \frac{2v}{nT} \left[-(\cos n\pi - 1) + (\cos 2n\pi - \cos n\pi) \right] \\
 &\quad \left[-\cos n\pi + 1 + 1 - \cos n\pi \right]
 \end{aligned}$$

~~AN~~ $\frac{(2 - 2\cos n\pi)}{n\pi}$

$$\frac{2v}{n\pi} \left(1 - \cos n\pi \right)$$

→ Exponential Series of,

$$f(t) = a_0 + \epsilon [a_n \cos \omega t + b_n \sin \omega t].$$

$$= a_0 + \frac{\epsilon}{\omega} \left[e^{j\omega t} \right]$$

$$= a_0 + a_n \left(\frac{e^{j\omega t} + e^{-j\omega t}}{2j} \right)$$

$$+ b_n \left(\frac{e^{j\omega t} - e^{-j\omega t}}{2j} \right)$$

$$= a_0 + \sum_{n=1}^{\infty} \left[e^{j\omega t} \left(\frac{a_n - jb_n}{2} \right) + e^{-j\omega t} \left(\frac{a_n + jb_n}{2} \right) \right]$$

$$\therefore f(t) = A_0 + \epsilon \left[A_n e^{j\omega t} + B_n e^{-j\omega t} \right].$$

where, $A_0 = a_0$


$$A_n = \frac{a_n - jb_n}{2}$$

$$A_{-n} = \frac{a_n + jb_n}{2}$$

$$B_n = \frac{a_n + jb_n}{2}$$

$$B_{-n} = \frac{a_n - jb_n}{2}$$
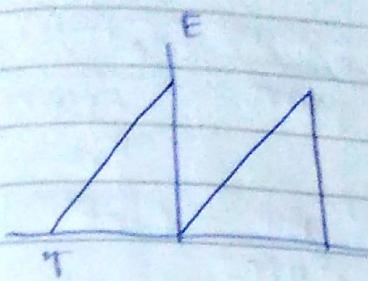
$$A_n = \frac{1}{T} \int_{-\infty}^{\infty} f(t) e^{-j\omega t} dt.$$



$$f(t) = \frac{E}{T} t \quad (0 < t < T)$$

$$\begin{aligned} A_0 = a_0 &= \frac{1}{T} \int_0^T f(t) \cdot dt \\ &= \frac{1}{T} \int_0^T \frac{E}{T} t \cdot dt \\ &= \frac{E}{T^2} \int_0^T t \cdot dt \\ &= E/T^2 \left(\frac{t^2}{2} \right)_0^T \\ &= E/T^2 \cdot \frac{T^2}{2} \end{aligned}$$

$$\therefore A_0 = E/2$$

$$\begin{aligned} a_n - j b_n &= \frac{1}{T} \int_0^T f(t) \cdot e^{-j n \omega t} \cdot dt \\ &= \frac{1}{T} \int_0^T \frac{E}{T} t \cdot e^{-j n \omega t} \cdot dt \\ &= \frac{E}{T^2} \int_0^T t \cdot e^{-j n \omega t} \cdot dt \\ &\Rightarrow E/T^2 \left[\left(e^{-j n \omega t} \cdot \int t \cdot dt \right)_0^T - \int_0^T e^{-j n \omega t} \cdot dt \right] \\ &= E/T^2 \left[\left(t \cdot \frac{e^{-j n \omega t}}{-j n \omega} \right)_0^T - \int_0^T \frac{e^{-j n \omega t}}{-j n \omega} \cdot dt \right] \\ &= E/T^2 \left[\frac{e^{-j n \omega T} \cdot T}{-j n \omega} + \frac{1}{j n \omega} \cdot \left(\frac{e^{-j n \omega t}}{-j n \omega} \right)_0^T \right] \end{aligned}$$

$$= E_T^2 \left[\frac{\bar{e}^{j\omega nT \cdot T}}{-j\omega n} + \frac{1}{j\omega n} \left(\frac{\bar{e}^{-j\omega nT} - 1}{-j\omega n} \right) \right]$$

$$= E_T^2 \left[\frac{\bar{e}^{j\omega nT \cdot T}}{-j\omega n} - \frac{1}{j^2 \omega^2 n^2} (\bar{e}^{j\omega nT} - 1) \right]$$

$$\therefore A_n = E_T^2 \left[\frac{\bar{e}^{j\omega nT \cdot T}}{-j\omega n} + \frac{1}{\omega^2 n^2} (\bar{e}^{j\omega nT} - 1) \right].$$

$$A_n = A_n + A_n \quad (\because A_n = a_n - j b_n)$$

and $b_n = j (A_m - A_n)$. $A_m = \frac{a_n + j b_n}{2}$

$$A_n = \frac{E}{\left(\frac{2\pi}{\omega}\right)^2} \left[\frac{\bar{e}^{\left(\frac{2\pi}{\omega}\right) j\omega n \left(\frac{2\pi}{\omega}\right)}}{-j\omega n} \cdot \frac{2\pi/\omega}{-j\omega n} + \frac{1}{\omega^2 n^2} \left(e^{-jn(2\pi)} - 1 \right) \right]$$


$$= \frac{E \omega^2}{4\pi^2} \left[\frac{\bar{e}^{\frac{4\pi^2 n}{\omega}} \cdot 2\pi}{-j\omega^2 n} + \frac{1}{\omega^2 n^2} \left(\bar{e}^{-jn(2\pi)} - 1 \right) \right]$$

$$A_n = \frac{jE}{2\pi n}$$

$$a_n = A_n + A_n = \frac{jE}{2\pi n} + \frac{jE}{2\pi(-n)} = 0$$

$$b_n = j(A_n - A_n) = j \left(\frac{je}{2\pi n} - \frac{je}{2\pi(-n)} \right)$$
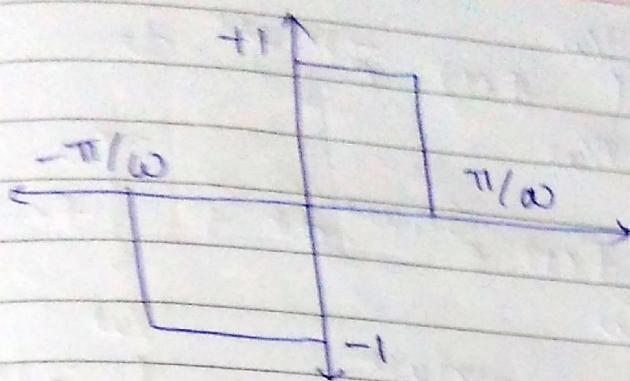
$$\therefore f(n) = a_0 + a_n \left(\frac{e^{j\omega nT} + e^{-j\omega nT}}{2j} \right) + b_n \left(\frac{e^{j\omega nT} - e^{-j\omega nT}}{2j} \right)$$



$$f(t) = \begin{cases} +1, & 0 < t < \pi/\omega \\ -1, & -\frac{\pi}{\omega} < t < 0 \end{cases}$$

$$\begin{aligned} A_0 = a_0 &= \frac{1}{T} \int_0^T f(t) \cdot dt \\ &= \frac{1}{T} \left[\int_{-\pi/\omega}^0 f(t) \cdot dt + \int_0^{\pi/\omega} f(t) \cdot dt \right] \\ &= \frac{1}{T} \left[\int_{-\pi/\omega}^0 -1 \cdot dt + \int_0^{\pi/\omega} 1 \cdot dt \right] \\ &= \frac{1}{T} \left[- (t) \Big|_{-\pi/\omega}^0 + (t) \Big|_0^{\pi/\omega} \right] \\ &= \frac{1}{T} \left[- (0 + \pi/\omega) + \pi/\omega \right] \\ &= \frac{1}{T} [\cancel{0}] \end{aligned}$$

$$= \cancel{\frac{2\pi}{\omega}} \cdot \cancel{\frac{\omega}{2\pi}}$$

$\therefore a_0 = 0$. (\because Area Under the curve = 0).

$$\begin{aligned}
 \text{and } A_n &= \frac{1}{T} \int_{-\pi/\omega}^{\pi/\omega} f(t) \cdot e^{-j\omega n t} dt \\
 &= \frac{1}{T} \left[\int_{-\pi/\omega}^0 f(t) \cdot e^{-j\omega n t} dt + \int_0^{\pi/\omega} f(t) \cdot e^{-j\omega n t} dt \right] \\
 &= \frac{1}{T} \left[\int_{-\pi/\omega}^0 -e^{-j\omega n t} dt + \int_0^{\pi/\omega} e^{-j\omega n t} dt \right] \\
 &= \frac{1}{T} \left[-\frac{(-e^{-j\omega n \pi}) - (-e^{j\omega n \pi})}{-j\omega n} + \frac{(e^{-j\omega n \pi}) - (e^{j\omega n \pi})}{j\omega n} \right] \\
 &= \frac{1}{T} \left[-\frac{(1 - e^{-j\omega n \pi})}{-j\omega n} + \frac{e^{-j\omega n \pi} - 1}{-j\omega n} \right] \\
 &= \frac{1}{T} \left[\cancel{-\frac{1 - e^{j\omega n \pi}}{j\omega n}} + \frac{e^{-j\omega n \pi} - 1}{j\omega n} \right] \\
 &= \frac{1}{T(j\omega n)} \left[\cancel{1 - e^{j\omega n \pi}} + \cancel{e^{-j\omega n \pi} - 1} \right] \\
 &= -\frac{2}{T(j\omega n)} \left[\frac{e^{j\omega n \pi} - e^{-j\omega n \pi}}{2} \right], \\
 &= \frac{-2}{T\omega n} (\sin n\pi) \\
 &= \frac{-2}{\frac{2\pi}{\omega} \cdot \omega n} (\sin n\pi) \\
 &= -\frac{1}{\pi n} (\sin n\pi),
 \end{aligned}$$

	$a_m = A_m + \bar{A}_m$
$\frac{-2}{T\omega n} (\sin n\pi)$	$= -\frac{1}{\pi n} (\sin n\pi) + \frac{-1}{\pi(-n)} (-\sin n\pi)$
	$= -\frac{1}{\pi n} (\sin n\pi) - \frac{1}{\pi n} (\sin n\pi)$