

Network Concepts.

classmate


Date _____

Page _____


Energy Sources —

→ Energy Sources can be classified into two sources


(i) Independent E.S. —

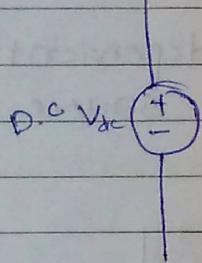


D.C V_{dc}

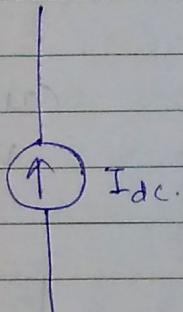

I_{dc}.

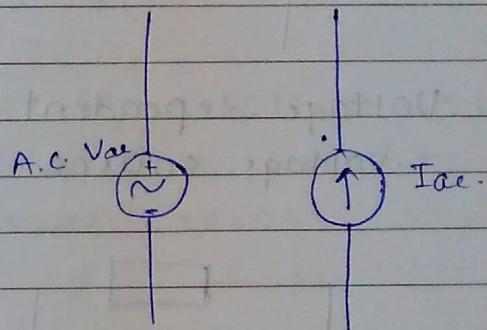

A.C V_{ac}

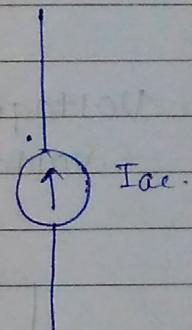


I_{ac}.


→ The elements in which the voltage is completely independent of current or the current is completely independent of the voltage elsewhere in the circuit.

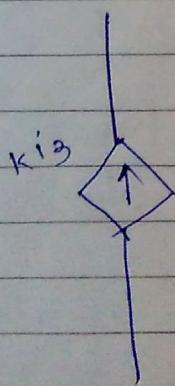(ii) Dependent E.S. —


→ The element in which the source quantity is determined by a voltage or a current existing at some other location in the system being analysed




current dependent
current source.

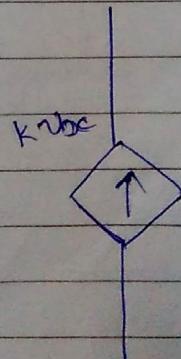

voltage dependent
current source.

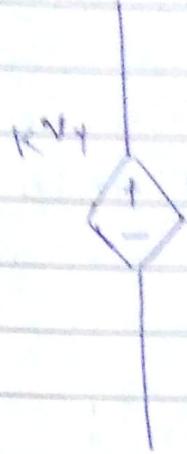


Voltage dependent
voltage source.

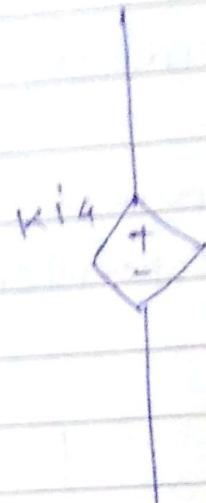

Current dependent
voltage source.

Ques.

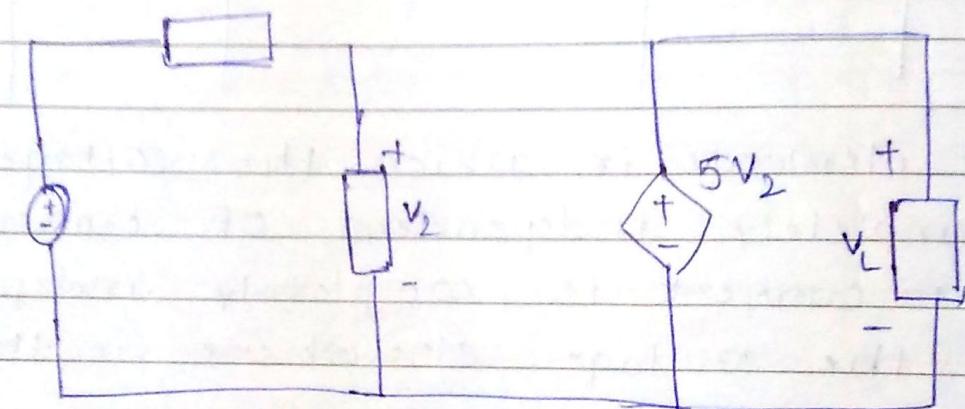


Here, $V_2 = 3V$, $V_L = ?$

Here, $5V_2 = V_L$

$$\therefore 5(3) = V_L$$

$$\therefore V_L = 15V.$$

⇒ Voltage Division rule -

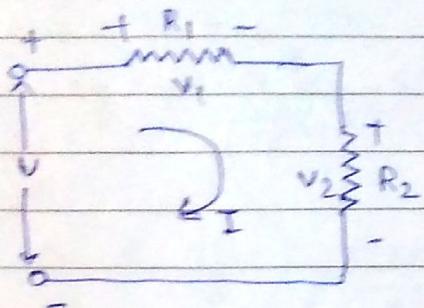

→ It is used to express the voltage across one of the several series resistors in terms of the voltage across the combination.


$$\text{Here } V = V_1 + V_2 \quad (\text{series})$$

$$\therefore V = IR_1 + IR_2$$

$$\therefore I = \frac{V}{R_1 + R_2} \quad \text{--- (1)}$$

$$\text{So, } V_1 = \frac{VR_1}{R_1 + R_2}, \quad V_2 = \frac{VR_2}{R_1 + R_2}$$

⇒ Current Division rule -

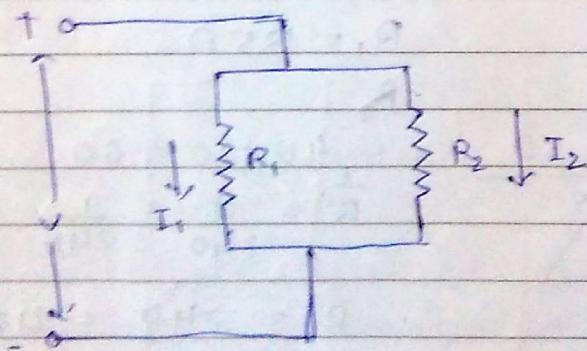

→ It is used to express the current flowing through one of the several resistors connected in parallel in term of the total current

$$I = I_1 + I_2$$

$$= \frac{V}{R_1} + \frac{V}{R_2}$$


$$\therefore I = V \left(\frac{R_1 + R_2}{R_1 R_2} \right)$$

$$\therefore V = \left(\frac{R_1 R_2}{R_1 + R_2} \right) I.$$

$$\text{So, } I_1 = \frac{I}{R_1} \left(\frac{R_1 R_2}{R_1 + R_2} \right)$$

$$\therefore I_1 = \frac{I R_2}{R_1 + R_2}, \quad I_2 = \frac{I R_1}{R_1 + R_2}.$$

Ques.

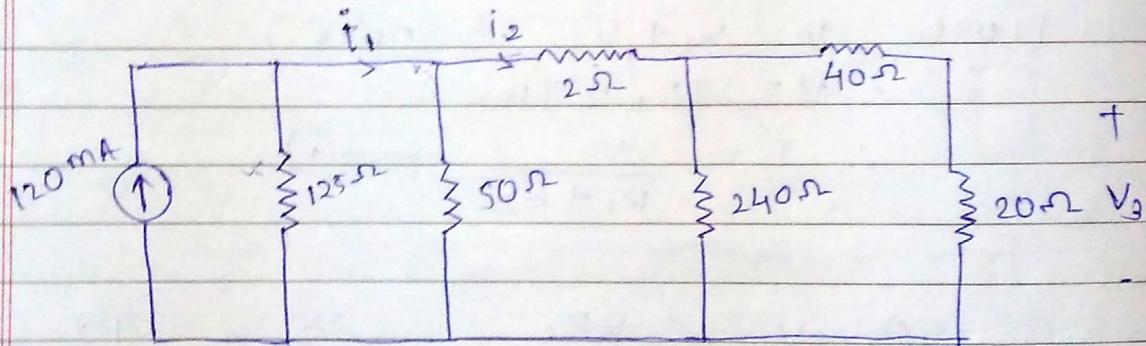

$$\text{Here } i = i_1 + i_2.$$

$$\text{and } i = 120 \text{ mA.}$$

~~$$i_1 = \frac{I R_2}{R_1 + R_2}$$~~

$$R_1 = 125 \Omega.$$

~~$$= \frac{120 \times 50}{175}$$~~

$$R_2 = 40 + 20 = 60$$

~~$$= \frac{600}{175}$$~~

$$R' = \frac{40}{240} + \frac{1}{240} = \frac{5}{240}$$

$$\therefore R_1 = \frac{48}{5} = 48 \Omega + 2 = 50$$


$$R'' = \frac{1}{50} + \frac{1}{50} = \frac{2}{50}$$

$$\therefore R' = 25 \Omega = R_2$$

$$\text{I}_1 = \frac{120 \times 125}{150}$$

$\therefore i_1 = \frac{120 \times 125}{150} = 100 \text{ mA.}$
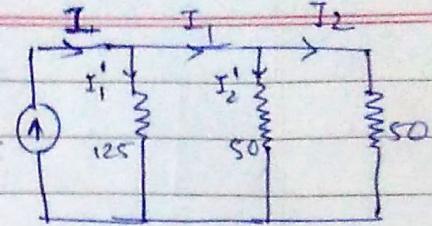
$$\text{and } i_2 = \frac{120 \times 50}{50 + 50}$$




$$I_1' = \frac{120 \times 25}{150} = 20 \text{ mA.}$$

$$\therefore I_1 = 120 - 20 = 100 \text{ mA.}$$

$$\text{and } I_2' = \frac{100 \times 50}{100} = 50 \text{ mA.}$$

$$\therefore I_2 = 50 - 50 = 50 \text{ mA.}$$

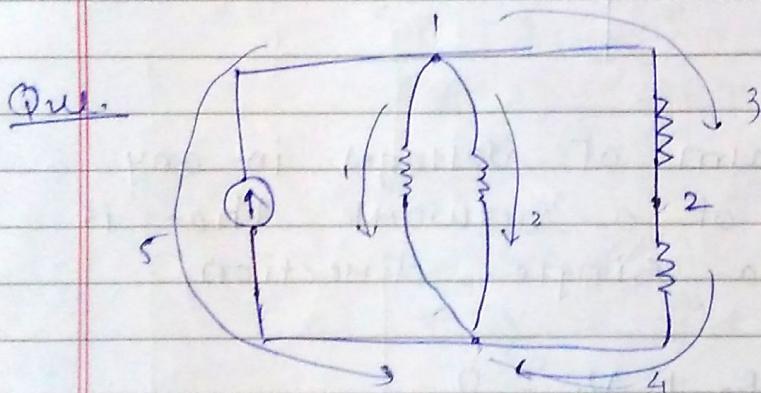⇒ Branch - A single path in a network composed of one element and the nod at each end of the element.




No. of paths = 5

No. of closed loops = 6


⇒ Kirchhoff's current law -

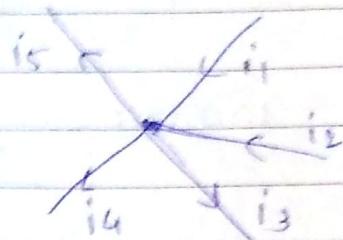→ The Algebraic sum of currents at any nod of a circuit is zero



$$i_1 + i_2 = i_3 + i_4 + i_5$$

→ Kirchhoff's Voltage Law -

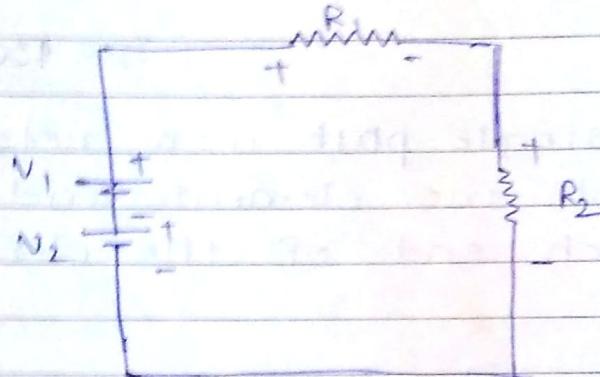


→ The Algebraic Sum of voltages in any closed path of a network that is traversed in a single direction.

$$V_1 - IR_1 - IR_2 + V_2 = 0$$

$$\therefore V_1 + V_2 = I(R_1 + R_2)$$

Ques.

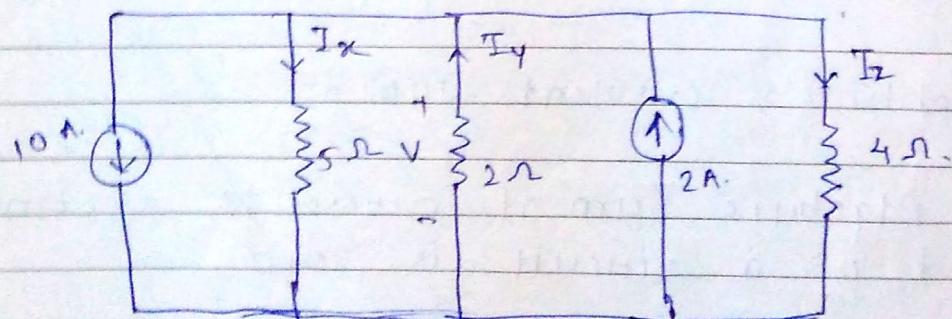

$$I_x = ?$$

$$V = ?$$

$$I_y = ?$$

$$I_z = ?$$

$$I_x + I_z + 10 = I_y + 2$$

$$\therefore I_x + I_z - I_y = -8 \quad \text{--- (1)}$$

$$V = I_x (5)$$

$$\therefore I_x = \frac{V}{5} \quad \text{--- (2)}$$

$$V = I_y (2)$$

$$\therefore I_y = \frac{V}{2} \quad \text{--- (3)}$$

$$V = I_z (4)$$

$$\therefore I_z = \frac{V}{4} \quad \text{--- (4)}$$

From eq. (1).

$$\therefore \frac{V}{5} + \frac{V}{4} + \frac{V}{2} = -8$$

$$\therefore \frac{8V + 10V + 20V}{40} = -8$$

$$\therefore \frac{38V}{40} = -8$$

$$\therefore \frac{V}{20} = -8$$

$$\therefore V = -8.42 \text{ V}$$

~~$$I_x = \frac{160}{5} = 32 \text{ A.}$$~~

$$I_x = -\frac{8.42}{5} = -1.68 \text{ A.}$$


~~$$I_y = \frac{160}{10} = 80 \text{ A.}$$~~

$$I_y = \left(\frac{-8.42}{2} \right) = -4.21 \text{ A.}$$

~~$$I_z = \frac{160}{4} = 40 \text{ A.}$$~~

$$I_z = -\frac{8.42}{4} = -2.105 \text{ A.}$$

Que.

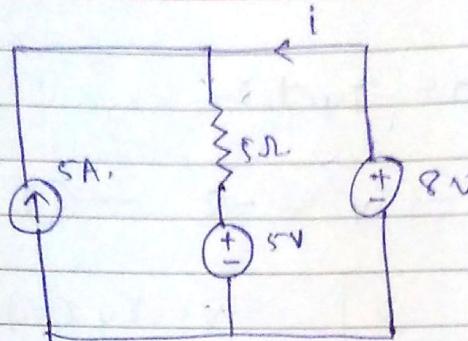

$$8 - 5 = i(5)$$



$$\therefore i(5) = 3$$

$$(i+5)5 = 3$$

$$\therefore i+5 = 0.6$$

$$\therefore i = -4.4 \text{ A.}$$

Que.

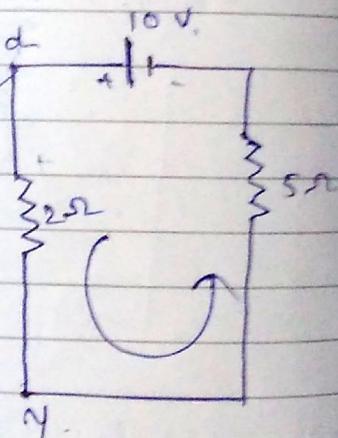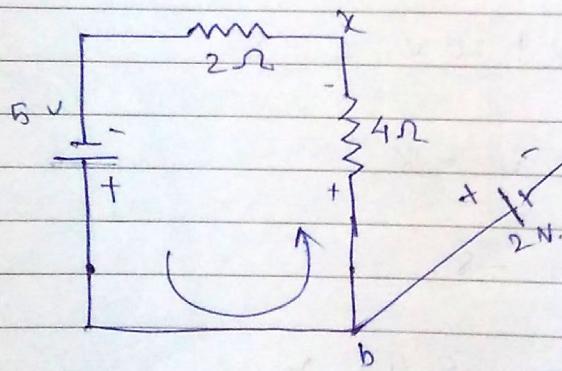

find V_{xy} ?

$$V_{xy} = V_{xb} + V_{bd} + V_{dy} \quad \text{--- (1)}$$

KVL for loop-1

$$5 - 4i_1 - 2i_1 = 0$$

$$\therefore 5 - 6i_1 = 0$$

$$\therefore 5 = 6i_1 \quad \text{--- (1)}$$

$$\therefore i_1 = \frac{5}{6} \text{ A.}$$

$$\therefore V_{bx} = 4i_1 = 4\left(\frac{5}{6}\right) = 3.33 \text{ V.}$$

KVL for loop-2

$$10 - 7i_2 = 0$$

$$\therefore \frac{10}{7} = i_2$$


$$\therefore i_2 = 1.428 \text{ A.}$$

$$57 \text{ V.}$$

$$\text{so, } V_{xy} = -3.33 + 2 + 2.857$$

$$\therefore V_{xy} = 1.527 \text{ V.}$$

Ques.

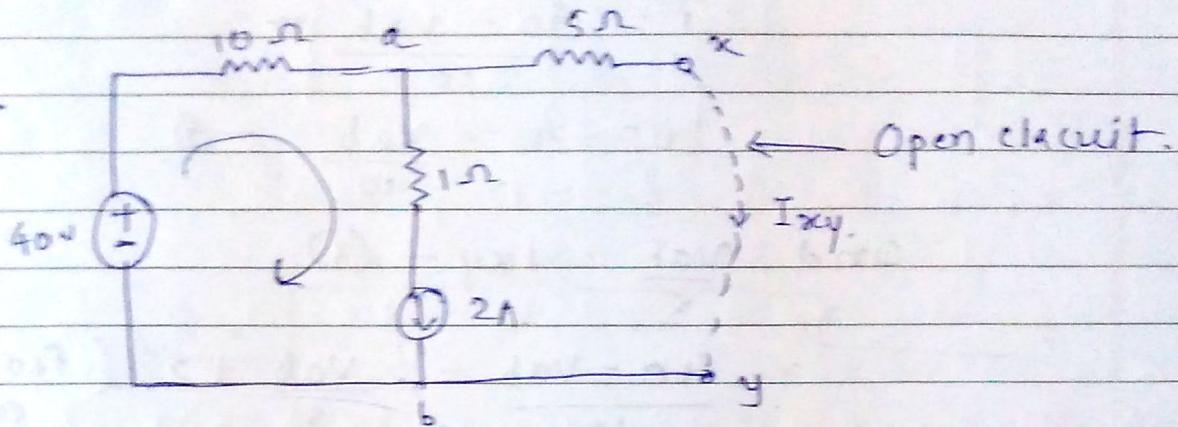

→ ~~if~~ find I_{xy} and V_{xy} —

~~if~~

$$40 - 10(2) - 1(2) = 0.$$

∴

$$40 - 10(2) = V_a.$$

$$\therefore V_a = 20 \text{ V.}$$

$$40 - V_{ab} = 10i$$

$$\therefore 40 - V_{ab} = 20.$$


$$V_b = -40 \text{ V}$$

$$\therefore V_{ab} = 20 \text{ V.}$$

$$\text{so, } V_{ab} = V_a - V_b \\ = 60 \text{ V.}$$

$I_{xy} = 0$. (open circuit)

(ii) Now x & y are connected —

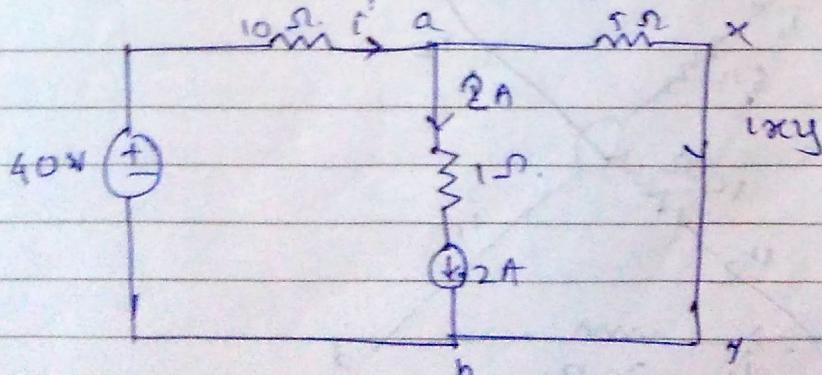

57 V.

$$\therefore i = i_{xy} + 2 \quad \text{--- (1)}$$

$$\text{and } 40 = 10i + V_{ab}$$

$$\therefore i = \frac{40 - V_{ab}}{10} =$$

$$\therefore i = 4 - \frac{V_{ab}}{10} \quad \text{--- (2)}$$

$$\text{and } \frac{V_{ab}}{5} = i_{xy} \quad \text{--- (3)}$$

$$\therefore \frac{40 - V_{ab}}{10} = \frac{V_{ab}}{5} + 2 \quad (\text{from eq-2})$$


$$\therefore 4 - \frac{V_{ab}}{10} = 2\frac{V_{ab}}{5} + 2$$

$$\therefore 2 = 3 \frac{V_{ab}}{10}$$

$$\therefore V_{ab} = 6.66 \text{ V.}$$

$$I_{xy} = \frac{6.66}{5} = 1.33 \text{ A.}$$

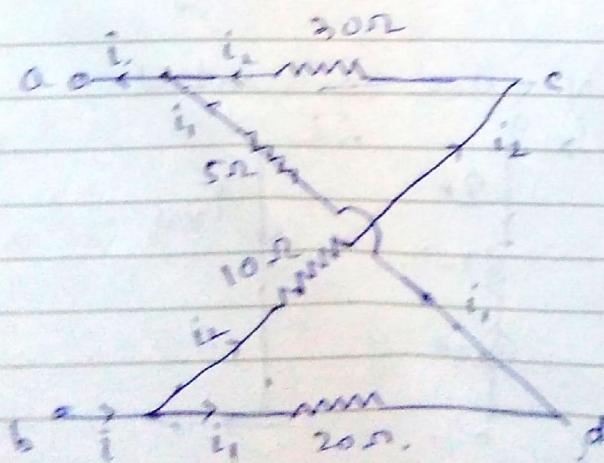Ques. find V_{ab} so that the voltage across 10Ω resistor is 45V also find the drop across 5Ω resistor




$$i_2 = \frac{45}{10} = 4.5 \text{ A.}$$

$$\text{and } V_L = 30(4.5) = 135 \text{ V}$$

$$\text{and } V = V_L + v_L \\ = 45 + 135$$

$$\therefore V = 180 \text{ V}$$

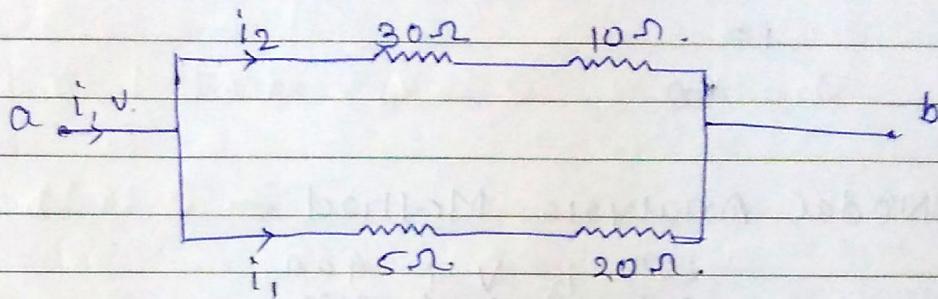

$$R_T = \frac{(40)(25)}{40+25} = \frac{1000}{65} = 15.38 \Omega$$


$$\text{so, } i = \frac{V}{R_T} = \frac{180}{15.38} \text{ A}$$

$$\therefore i = 11.7 \text{ A.}$$

$$\text{so, } i_1 = 7.2 \text{ A.}$$

$$\text{so, } V_5 = i_1(5)$$

$$\therefore V_5 = 36 \text{ V.}$$

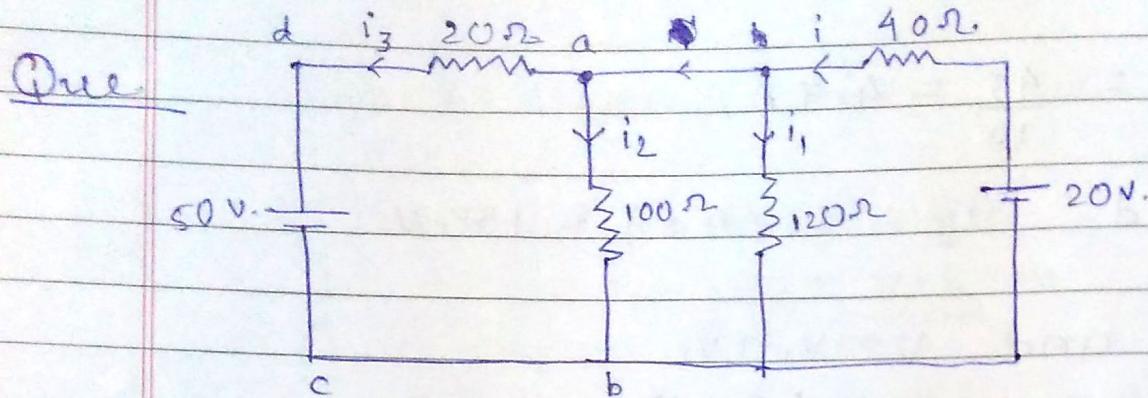


→ At b-node, for loop abcd,

\Rightarrow

50

⇒ Nodal Analysis Method —

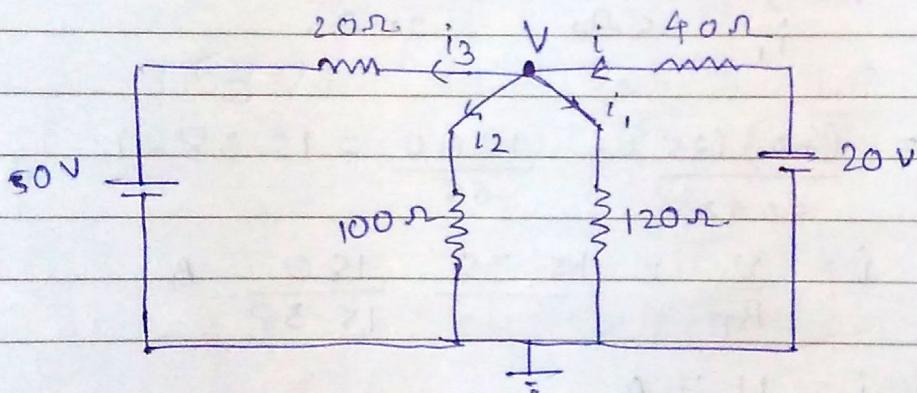

$$\frac{20 - V}{40} = \frac{V}{120} + \frac{V}{100} + \frac{V - 50}{20}$$

$$\therefore 0.5 - \frac{V}{40} = \frac{V}{120} + \frac{V}{100} + \frac{V}{20} - 2.5$$

$$\therefore 3 = \frac{V}{120} + \frac{V}{100} + \frac{V}{20} + \frac{V}{40}$$

$$\therefore \underline{V = 32V}$$

$$i_r = i_1 + i_2 + i_3.$$


$$\text{so, } i_1 = \frac{V}{120} = \frac{32}{120} = 0.266 \text{ A.}$$

$$i_2 = \frac{V}{100} = \frac{32}{100} = 0.32 \text{ A.}$$

$$i_3 = \frac{V-50}{20} = -0.9 \text{ A}$$

$$\therefore i = -0.314 \text{ A}$$

Ques

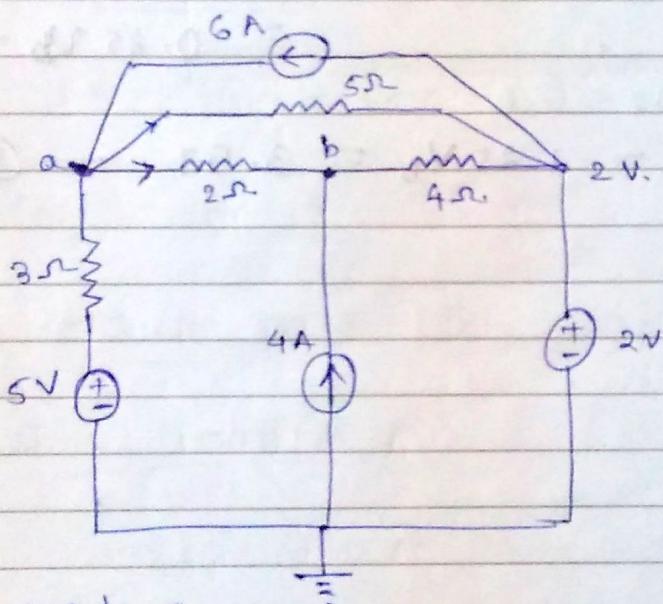

at particular node we have to assume them at higher potential

→ for node 'a',

$$\frac{V_a - 5}{3} + \frac{V_a - V_b}{2} + \frac{V_a - 2}{5} - 6 = 0. \quad \text{--- (1)}$$

→ for node 'b',

$$\frac{V_b - V_a}{2} + \frac{V_b - 2}{4} - 4 = 0 \quad \text{--- (2)}$$

→ solving eq. (1) and eq. (2),

$$\therefore \frac{V_a - 5}{3} + \frac{V_a - V_b}{2} + \frac{V_a - 2}{5} = 6$$

$$= \frac{V_b - V_a}{2} + \frac{V_b - 2}{4} - 4 = 0$$


$$\therefore 2\left(\frac{V_a - V_b}{2}\right) + \frac{V_a - 5}{3} + \frac{V_a - 2}{5} = \frac{V_b - 2}{4} + 2$$

$$\therefore V_a - V_b + 0.33V_a - 1.67 + 0.2V_a - 0.4 \\ = 0.25V_b - 0.5 + 2$$

$$\therefore 1.58V_a - 1.25V_b = 3.57 \quad \text{--- (3)}$$

⇒ Mess analysis method —

Ques

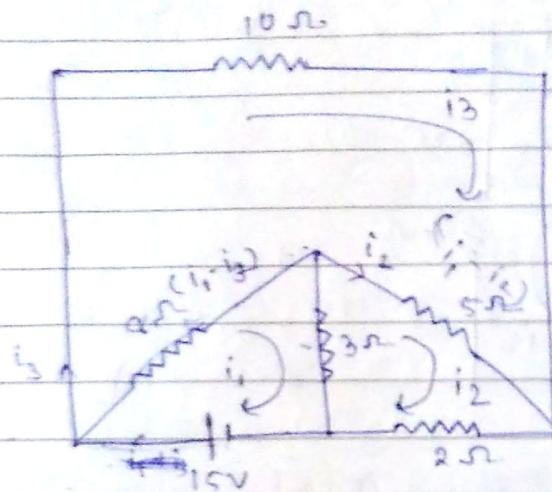

i_1, i_2 and i_3
are not branch currents.
They are loop currents.

for loop - 1

$$15 - 8(i_1 - i_3) - 3(i_1 - i_2) = 0. \quad \text{--- (1)}$$

for loop - 2

$$-3i_1 + 10i_2 - 5i_3 = 0 \quad \text{--- (2),}$$


for loop - 3

$$-8i_1 - 5i_2 + 23i_3 = 0. \quad \text{--- (3).}$$

$$\therefore i_1 = 2.63 \text{ A}$$

$$\therefore i_2 = 1.4 \text{ A}$$

$$\therefore i_3 = 1.22 \text{ A}$$

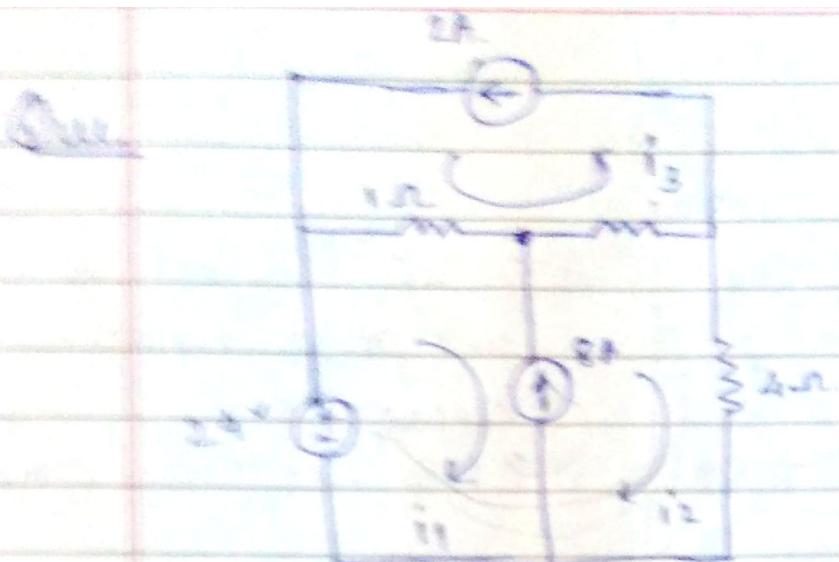


$P_{mn} = ?$

→ Here. $i_3 = 2A$.

$$i_2 - i_1 = 8A$$

Ques-

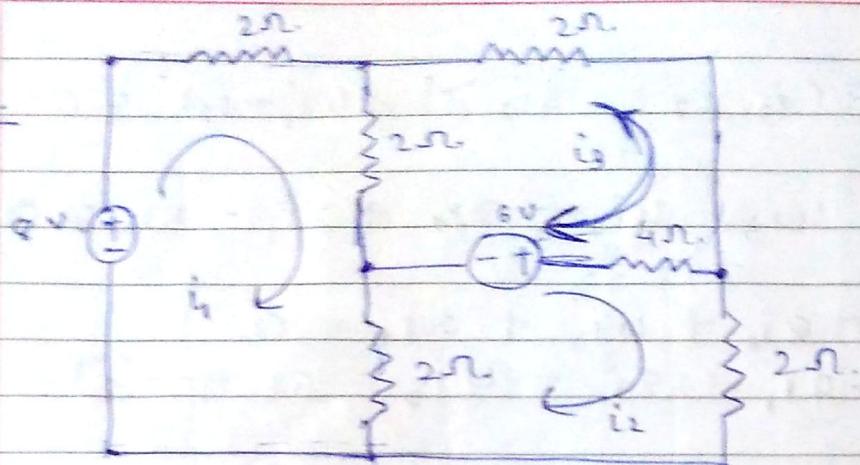

$$I_{4\Omega} = ?$$

$$\begin{aligned} -8 + 2(i_1 - i_2) + 2(i_1 - i_3) + 2i_1 &= 0 \\ \therefore -8 + 2i_1 - 2i_2 + 2i_1 + 2i_3 + 2i_1 &= 0 \\ \therefore -8 + 6i_1 - 2i_2 + 2i_3 &= 0 \end{aligned}$$

$$\therefore 6i_1 - 2i_2 + 2i_3 = 8 \quad \text{--- (1)}$$

$$\begin{aligned} 6 + 4(-i_2 - i_3) - 2i_2 + 2(i_1 - i_2) &= 0 \\ \therefore 6 + 4i_2 + 4i_3 - 2i_2 + 2i_1 - 2i_2 &= 0 \\ \therefore 2i_1 + 4i_3 &= -6 \quad \text{--- (2)} \end{aligned}$$

$$6 = 4(i_2 + i_3)$$

$$\begin{aligned} \therefore -8i_2 - 4i_3 + 2i_1 + 6 &= 0 \\ \therefore 8i_2 + 4i_3 - 2i_1 &= 6 \quad \text{--- (2).} \end{aligned}$$

$$\begin{aligned} -8 + 2(i_1 - i_2) + 2(i_1 - i_3) + 2i_1 &= 0 \\ \therefore -8 + 2i_1 - 2i_2 + 2i_1 - 2i_3 + 2i_1 &= 0 \end{aligned}$$

$$\therefore -8 + 6i_1 - 2i_2 - 2i_3 &= 0$$

$$\therefore 6i_1 - 2i_2 - 2i_3 = 8 \quad \text{--- (1)}$$

$$\rightarrow 6 + 4(i_3 - i_2) - 2i_2 + 2(i_1 - i_2) = 0.$$

$$\therefore 6 + 4i_3 - 4i_2 - 2i_2 + 2i_1 - 2i_2 = 0$$

$$\therefore 6 - 8i_2 + 4i_3 + 2i_1 = 0$$


$$\therefore -2i_1 + 8i_2 - 4i_3 = 6 \quad \text{--- (1)}$$

$$\rightarrow 6 + 4(i_3 - i_2) + 2i_3 + 2(i_2 - i_1) = 0.$$

$$\therefore 6 + 4i_3 - 4i_2 + 2i_3 + 2i_2 - 2i_1 = 0$$

\therefore

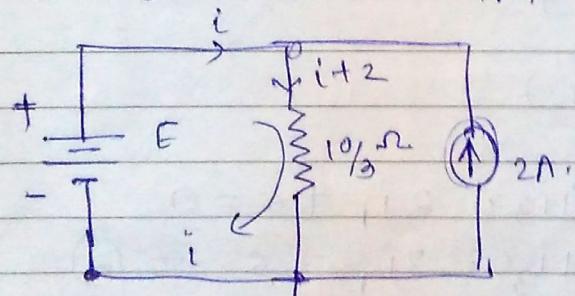Ques find the value of E if the power supplied by the current source is double that of the supplied by the battery.



\rightarrow Here, power supplied by battery $P = VI$
 $= E(i)$.

and power supplied by current, $= E(2)$

$$\therefore 2[Ei] = E(2).$$

$$\therefore i=1 \quad \text{--- (1)}$$


$$E - \frac{10}{3}(i_1) = 0.$$

$$\therefore E = \frac{10}{3}(i_1 + 2)$$

$$= \frac{10}{3}(3)$$

$$\therefore E = 10V$$

Ques.

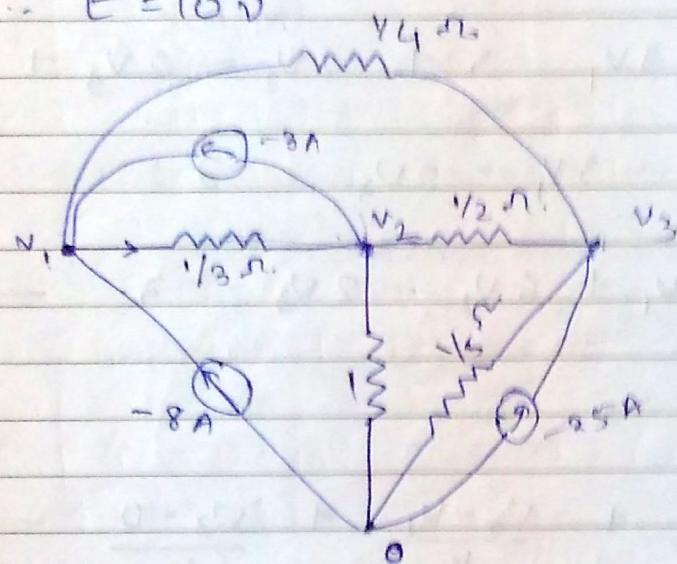

KCL at node v_1 ,

$$\frac{v_1 - v_2}{1} - (-8) - (-3) + \frac{v_1 - v_3}{1/4} = 0$$

$$\therefore 3(v_1 - v_2) + 11 + 4(v_1 - v_3) = 0$$

$$\therefore 3v_1 - 3v_2 + 4v_1 - 4v_3 + 11 = 0$$

$$\therefore 7v_1 - 3v_2 - 4v_3 = -11 \quad \text{--- (1)}$$

→ at node v_2 ,

$$\frac{v_2 - v_1}{Y_3} - 3 + \frac{v_2 - v_3}{Y_2} + \frac{v_2 - 0}{1} = 0$$

$$\therefore 3(v_2 - v_1) - 3 + 2(v_2 - v_3) + v_2 = 0$$

$$\therefore 3v_2 - 3v_1 - 3 + 2v_2 - 2v_3 + v_2 = 0$$

$$\therefore 6v_2 - 3v_1 - 2v_3 = 3$$

$$\therefore -3v_1 + 6v_2 - 2v_3 = 3 \quad \text{--- (2)}$$

→ at node v_3 ,

$$\frac{v_3 - v_2}{Y_2} + \frac{v_3 - v_1}{Y_4} + \frac{v_3 - 0}{Y_5} - (-25) = 0$$

$$\therefore 2(v_3 - v_2) + 4(v_3 - v_1) + 5(v_3) = -25$$

$$\therefore 2v_3 - 2v_2 + 4v_3 - 4v_1 + 5v_3 = -25$$


$$\therefore 11v_3 - 4v_1 - 2v_2 = -25$$

$$\therefore 4v_1 + 2v_2 - 11v_3 = 25 \quad \text{--- (3)}$$

$$v_1 = -6.85 \text{ V}$$

$$v_2 = -4.8 \text{ V}$$

$$v_3 = -5.63 \text{ V}$$

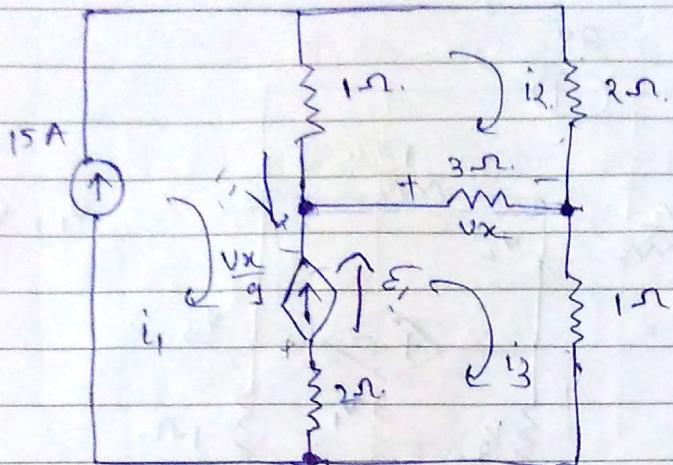Ques.

$$\text{for supernode, } i_1 = 15 \quad \textcircled{1}$$

$$V_x = 3(i_2 - i_3) \quad \textcircled{2}$$



$$\frac{V_x}{9} = i_3 - i_1 \quad \textcircled{3}$$

$$i_2 + 2i_3 = 45 \quad \textcircled{4} \quad (\because \text{by putting } V_x \text{ in eq. (3)})$$

$$6i_2 - 3i_3 = 15 \quad \textcircled{5}$$

$$i_2 = 11 \text{ A}$$

$$i_3 = 17 \text{ A}$$

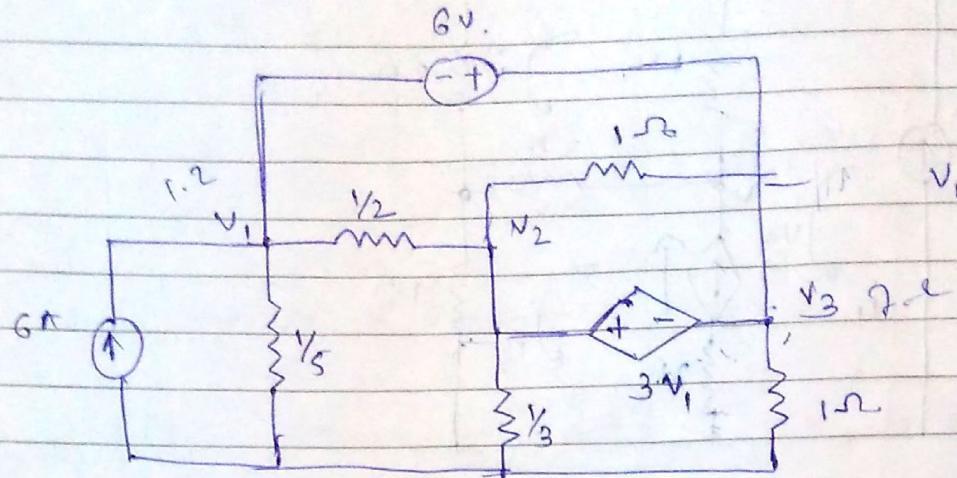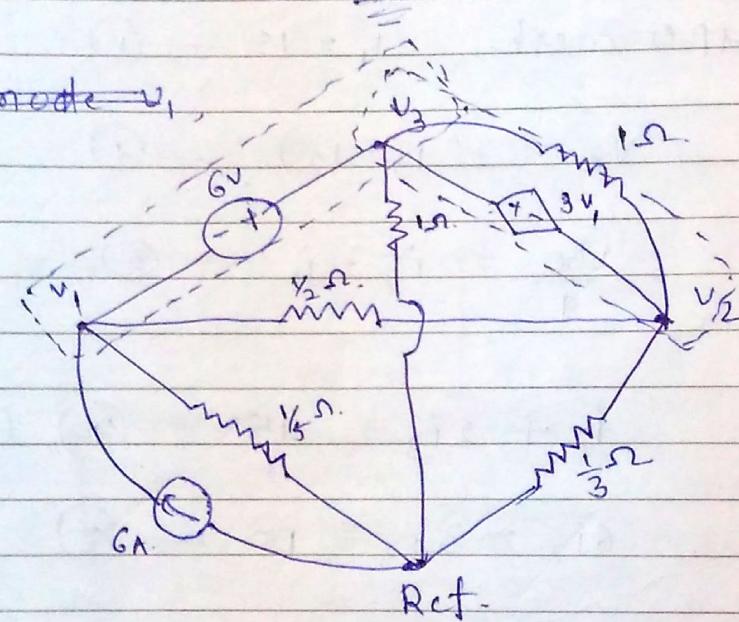Ques→ At node v_1 ,Example of Supernode.→ At node $1-3$,

$$\frac{v_1 - 0}{1/5} - 6 + \frac{v_1 - v_2}{1/2} + \frac{v_3}{1} = 0$$

$$\therefore 5v_1 - 2v_2 + v_3 = 6 \quad \text{--- (1)}$$

→ At node $3-2$,

$$\frac{v_2}{1/2} + \frac{v_2 - v_1}{1/2} + \frac{v_3}{1} = 0$$

$$\therefore -2v_1 + 5v_2 + v_3 = 0 \quad \text{--- (2)}$$

$$\rightarrow 3v_1 + v_2 - v_3 = 0 \quad \text{--- (3)}$$

$$\therefore v_1 = -0.59 \text{ V}$$

$$\therefore v_2 = 0.098 \text{ V}$$

$$\therefore v_3 = -1.692 \text{ V}$$

$$\begin{array}{c} \Delta \\ \text{G}_3 \end{array} \quad \begin{aligned} v_3 &= v_1 + \text{G}_3 \\ &= \text{G}_3 + \text{C} \end{aligned}$$


$$v_3 = 7.2 \text{ V}$$

$$Sp = 3.6$$


$$7.2 + 3.6$$

$$= 10.8$$

Ques.

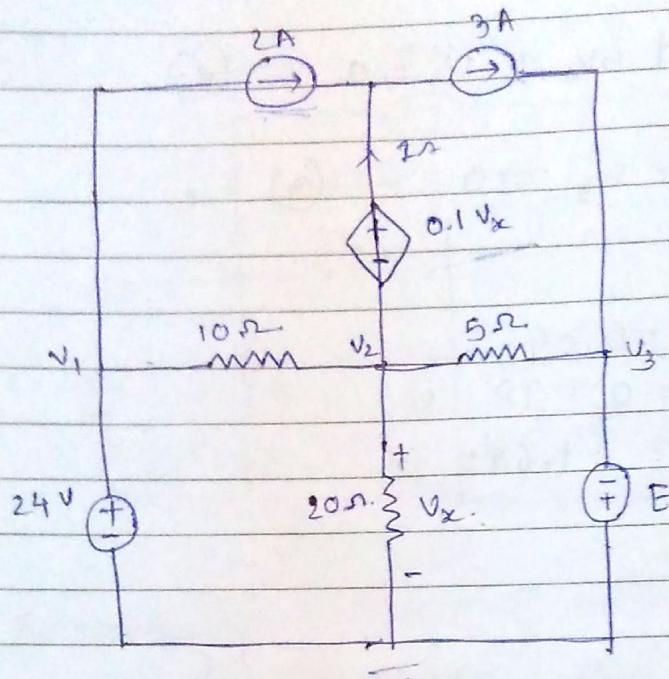

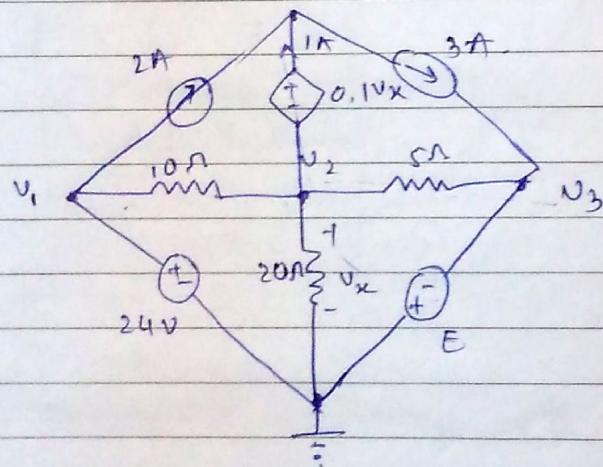→ Using Node analysis determine the value of E , which causes V_x to be zero.



→ Set node V_2 , ($V_2 = V_x$)

$$V_1 = 24 \quad \frac{V_x - V_1}{10} + \frac{V_x - V_3}{5} + \frac{V_x - 0}{20} + \cancel{\frac{V_x - 0}{0.1}} = 0.$$

$$\therefore \frac{V_x - 24}{10} + \frac{V_x + E}{5} + \frac{V_x + 0}{20} = 0.$$

= 0.

$$\therefore \frac{V_x}{5} - 2.4 + \frac{V_x}{5} + E/5 + \frac{V_x}{20} = 0$$


$$\therefore 8 \frac{V_x}{20} + \frac{V_x}{20} + E/5 = 2.4$$

$$\therefore 9 \frac{V_x}{20} + E/5 = 2.4$$

$$\therefore E = 12V.$$

$$\therefore E = 7V. (\because V_x = 0).$$

Ques.

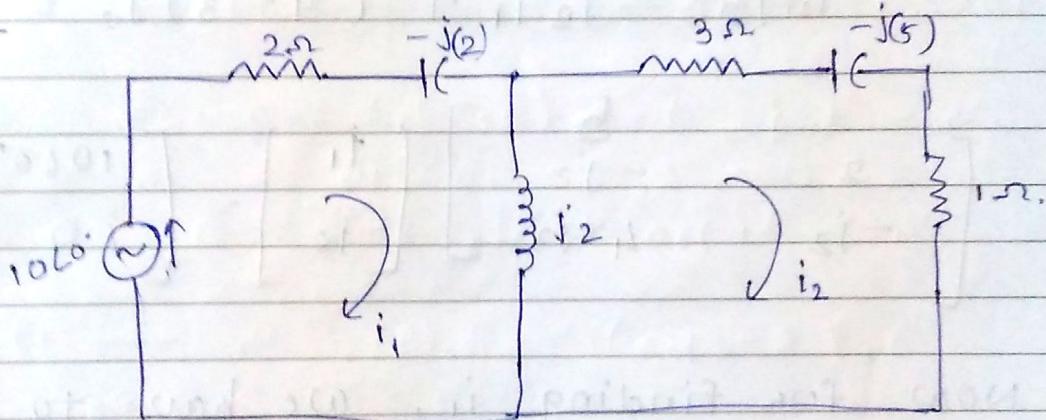

→ Using Mesh analysis,

$$10 - 2i_1 + i_1 j_2 + j_2(i_2 - i_1) = 0.$$

$$\therefore 10 - 2i_1 + i_1 j_2 + i_2 j_2 - i_1 j_2 = 0$$

$$\therefore 10 - 2i_1 + i_2 j_2 = 0. \quad \text{--- (1)}$$

$$\rightarrow -3i_2 + i_2 j_5 - i_2 + j_2(i_1 - i_2) = 0$$

$$= 0.$$

$$\therefore -3i_2 + i_2 j_5 - i_2 + i_1 j_2 - i_2 j_2 = 0.$$

$$= 0.$$

$$\therefore -4i_2 + i_2 j_5 + i_1 j_2 - i_2 j_2 = 0. \quad \text{--- (2)}$$

~~from eq.(1),~~

$$i_7 = \frac{10 + i_2 j_2}{2} \quad \text{--- (a)}$$

\rightarrow Putting the value of i_7 in eq.(2),

$$\therefore -4i_2$$

$$\therefore 4i_1 + i_2 j_2 - i_2 j_5 - i_1 j_2 = 0$$

$$\therefore \cancel{i_2} - j_2 i_1 + (4 - j_3) i_2 = 0. \quad \text{--- (b)}$$

$$\begin{bmatrix} 2 & -j_2 \\ -j_2 & 4 - j_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 10 \angle 0^\circ \\ 0 \end{bmatrix}$$

\rightarrow Now, for finding i_1 , we have to replace 1st column with voltage.

$$\text{so, } \left| \begin{array}{cc} 10 \angle 0^\circ & -j_2 \\ 0 & 4 - j_3 \end{array} \right| = i_1$$

$$\left| \begin{array}{cc} 2 & -j_2 \\ -j_2 & 4 - j_3 \end{array} \right|$$

$$\therefore i_1 = \frac{(10 \angle 0^\circ)(4 - j_3)}{(8 - 2j_3) - j_2^2} = \frac{40 \angle 0^\circ - (10 \angle 0^\circ) j_2}{8 - 2j_3 - j_2^2}$$

$$\therefore i_1 = \frac{(10 + 0j)(4 - j_3)}{(8 - 2j_3) - j_2^2} = \frac{41.23 (-14.03)}{(8 - 2j)^2 + 1} = \frac{41.23 (-14.03)}{9 - 2j} = \frac{41.23 (-14.03)}{9.22 (-12.52)}$$

→ for $i_2 =$

$$\begin{vmatrix} 2 & 10 \angle 0^\circ \\ -j_2 & 0 \end{vmatrix} \begin{vmatrix} 2 & -j_2 \\ -j_2 & 4 - j_3 \end{vmatrix}$$


$$i_1 = 3.7 \angle -10.22^\circ, \quad i_2 = 1.5 \angle -63^\circ$$

→ Power Supplied by the source -

$$P = VI \cos \theta.$$

$$= 10 \times 3.7 \times 0.984$$

$$\therefore P = 36.41 \text{ Watts.}$$

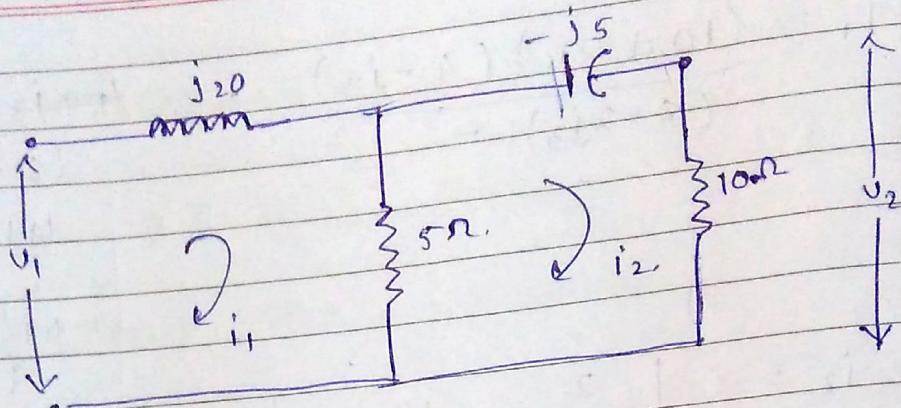Ques.

$$\frac{v_2}{v_1} = ?$$

→ for 1st Mesh -

$$v_1 - I_1 j_{20} + 5(I_2 - I_1) = 0.$$

$$\therefore v_1 - I_1 j_{20} + 5I_2 - 5I_1 = 0$$

$$\therefore I_1(5 + j_{20}) - I_2(5) = v_1 \quad \text{--- (1)}$$

→ for 2nd mesh -

$$v_2 + I_2 j_5 + 5(I_2 - I_1) + 10I_2 = 0.$$

$$\therefore 15I_2 - 5I_1 + I_2 j_5 = -v_2 \quad \text{--- (2)}$$

$$\begin{bmatrix} 5 + j_{20} & -5 \\ -5 & 15 + j_5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} v_1 \\ -v_2 \end{bmatrix}$$

$$\therefore I_1 = \begin{vmatrix} 5+j20 & v_1 \\ -5 & 0 \\ \hline s+j20 & -5 \\ -5 & 15-j5 \end{vmatrix}$$

$$\therefore I_2 = \frac{5v_1}{(5+j20)(15-j5) - 25}$$


$$\therefore I_2 = \frac{5v_1}{(76.65+10j) - 25} = \frac{5v_1}{75+300j-25j-100j^2}$$

$$\therefore I_2 = \frac{5v_1}{51.97-11.093} = \frac{5v_1}{150+j275}$$

$$\therefore I_2 = 0.096 \angle -11.093^\circ A.$$

and, $v_2 = 10I_2$. (from figure).

$$\therefore \frac{v_2}{v_1} =$$

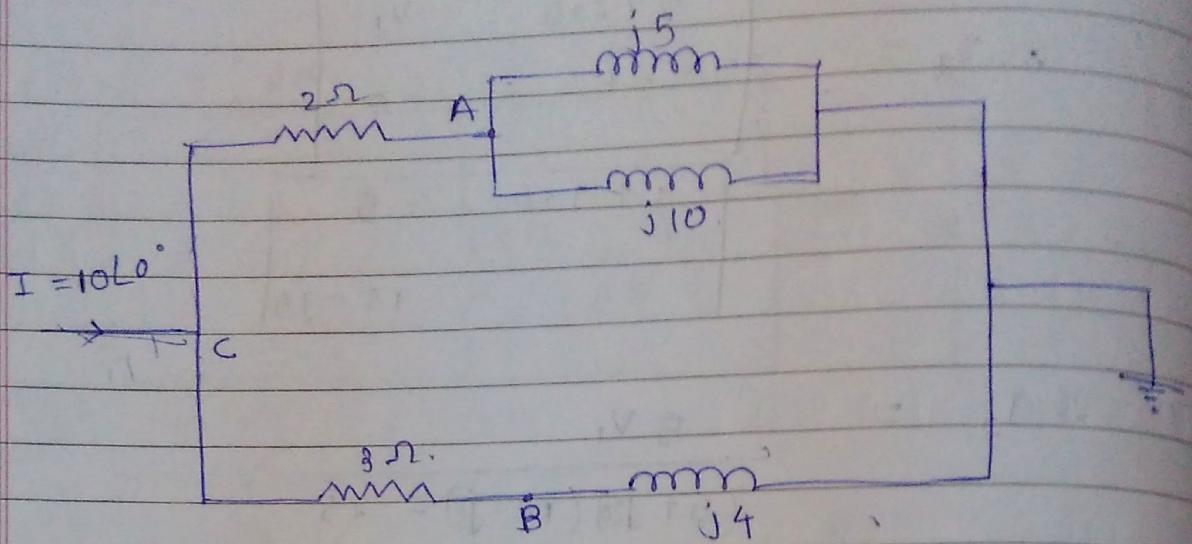Que.

$$V_{AB} = ?$$

Note, at node A,

~~$$\text{Resistor } R_A = \frac{j5 \cdot j10}{j5 + j10} = \frac{(5 \angle 90^\circ)(10 \angle 0^\circ)}{5 \angle 90^\circ + 10 \angle 0^\circ}$$~~

~~$$\therefore R_A = \frac{50 \times 180^\circ}{15 \angle 90^\circ}$$~~

~~$$\therefore R_A = 3.33 \angle 180^\circ$$~~

~~$$\therefore R_A = 0 + 3.33j$$~~


$$\rightarrow \text{Resistor } R_A = 2 + 3.33j \Omega$$

$$\rightarrow \text{And for B node, Register } R_B = 3 + 4j \Omega$$

$$R = \frac{(2 + 3.33j)(3 + 4j)}{(2 + 3.33j) + (3 + 4j)} = \frac{19.422 \angle 112.5^\circ}{8.872 \angle 55^\circ}$$

$$= 2.188 \angle 56.44^\circ$$

$$\therefore R = 1.21 + 1.824j$$

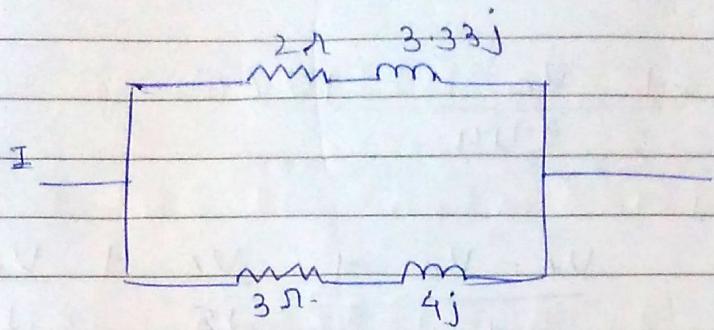

~~$$\text{so, } V = IR$$

$$= (10 \times 0') (2.188 \angle 56.44^\circ)$$

$$= 21.88 \angle 56.44^\circ$$~~

~~$$I_1 = \frac{V}{R_1}$$

$$= \frac{21.88 \angle 56.44^\circ}{2 + 3.33j}$$~~

~~$$\therefore I_1 = 5.632 \angle -2.57^\circ$$~~

~~$$I_2 = \frac{V}{R_2}$$

$$= \frac{21.88 \angle 56.44^\circ}{3 + 4j}$$~~

~~$$\therefore I_2 = 4.376 \angle 3.309^\circ$$~~

at point A, $V_A = 5.632 \times 2 = 11.264 \angle -2.57^\circ$

at

$$\text{At node C, } \frac{V_C - V_A}{2} + \frac{V_C}{3+j4} = 10 \text{ (1)}$$

$$\text{At node A, } \frac{V_A - V_C}{2} + \frac{V_A}{j5} + \frac{V_A}{j10} = 0$$

$$\rightarrow \therefore 0.5V_C - 0.5V_A + (0.12 - 0.16j)V_C = 10 \quad \text{(1)}$$

$$\therefore 0.5V_C - 0.5V_A + 0.12V_C - (0.16j)V_C = 0 \quad \text{(1)}$$

$$\therefore 0.62V_C - 0.5V_A - (0.16j)V_C = 10 \quad \text{(1)}$$

$$\therefore (0.62 - 0.16j)V_C - 0.5V_A = 10 \quad \text{(1)}$$

$$\rightarrow \underline{0.5V_A - 0.5V_C + (0 - 0.2j)V_A + (0 - 0.1j) = 0}$$

$$\therefore (0.5 - 0.3j)V_A - 0.5V_C = 0 \quad \text{(2)}$$

$$\begin{bmatrix} -0.5 & 0.62 - 0.16j \\ 0.5 - 0.3j & -0.5 \end{bmatrix} \begin{bmatrix} V_A \\ V_C \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix}$$

$$\therefore -0.25 - (0.5 - 0.3j)(0.62 - 0.16j)$$

$$\therefore V_A = \begin{vmatrix} 10 & 0.62 - 0.16j \\ 0 & -0.5 \\ -0.5 & 0.62 - 0.16j \\ 0.5 - 0.3j & -0.5 \end{vmatrix}$$

$$= -5$$


$$0.25 - (0.262 - 0.266j)$$

$$\therefore V_A = 19.777 \angle 87.41^\circ$$

$$\therefore V_B = 21.8 \angle 56.4^\circ$$

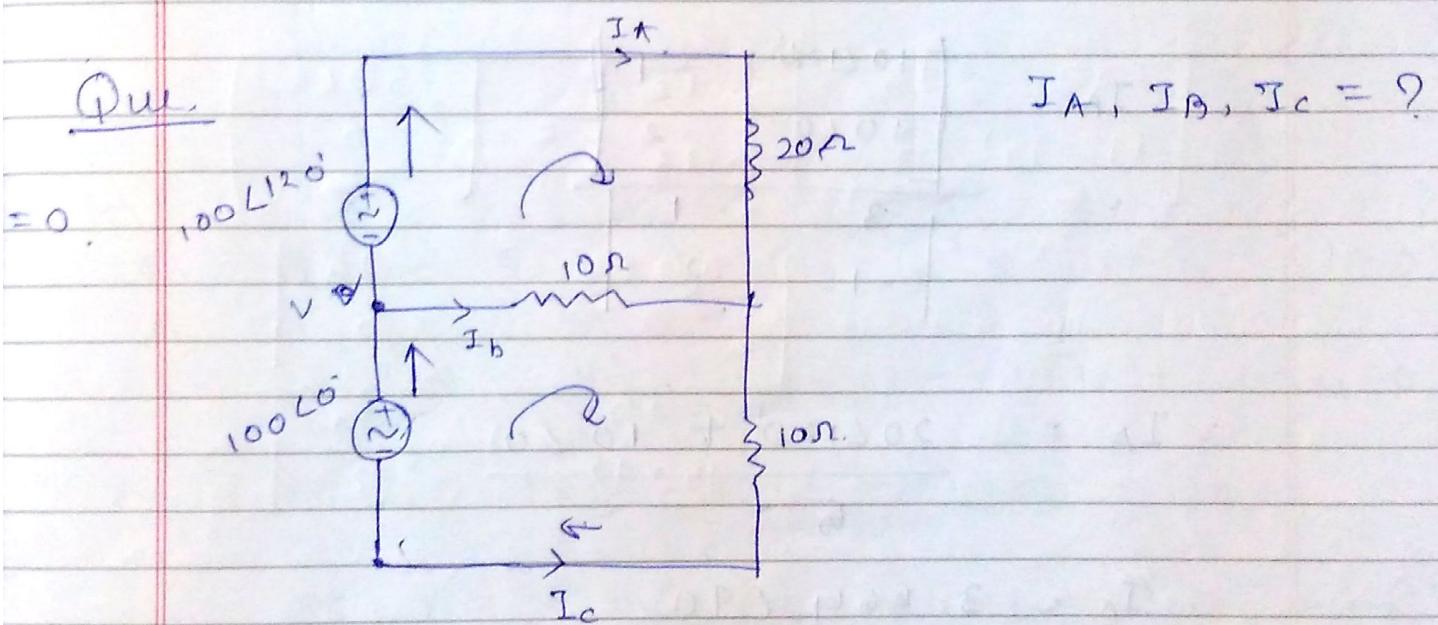Q1

$$\text{and } V_B = \frac{V_c \cdot j4}{(3 + j4)}$$



→ for first loop,

$$100\angle 120^\circ - 20I_A + 10(I_B - I_A) = 0$$

$$\therefore 100\angle 120^\circ = 20I_A - 10I_B + 10I_A$$

$$\therefore 100\angle 120^\circ = 30I_A - 10I_B$$

$$\therefore 10\angle 120^\circ = 3I_A - I_B \quad \text{--- (1)}$$

→ for loop - 2,

$$100 I_0 + 10(I_A - I_B) - 10 I_B = 0.$$

$$\therefore 100 = 20 I_B - 10 I_A$$

$$\therefore 10 = 2 I_B - I_A \quad \text{--- (2)}$$

$$\begin{bmatrix} 3 & -1 \\ -1 & 2 \end{bmatrix} \begin{bmatrix} I_A \\ I_B \end{bmatrix} = \begin{bmatrix} 10 \angle 120^\circ \\ 10 \angle 0^\circ \end{bmatrix}$$

$$\therefore I_A = \frac{\begin{vmatrix} 10 \angle 120^\circ & -1 \\ 10 \angle 0^\circ & 2 \end{vmatrix}}{\begin{vmatrix} 3 & -1 \\ -1 & 2 \end{vmatrix}}$$

$$\therefore I_A = \frac{20 \angle 120^\circ + 10 \angle 0^\circ}{5}$$

$$\therefore I_A = 3.464 \angle 90^\circ$$

$$\therefore I_B = \frac{\begin{vmatrix} 3 & 10 \angle 120^\circ \\ -1 & 10 \angle 0^\circ \end{vmatrix}}{\begin{vmatrix} 3 & -1 \\ -1 & 2 \end{vmatrix}}$$

$$= \frac{30 \angle 0^\circ + 10 \angle 120^\circ}{5} = 5.29 \angle 19.10^\circ$$

$$\text{and } I_C = 5 - I_B = 5.29 \angle 19.10^\circ$$

• 9°. A.

Ques

→


→

$$\rightarrow J_A + J_B + J_C = 0,$$

$$\therefore \frac{V + 100 \angle 120^\circ}{20} + \frac{V}{10} + \frac{V - 100 \angle 0^\circ}{10}$$

~~50 L₀~~ 5Ω.

Ques.

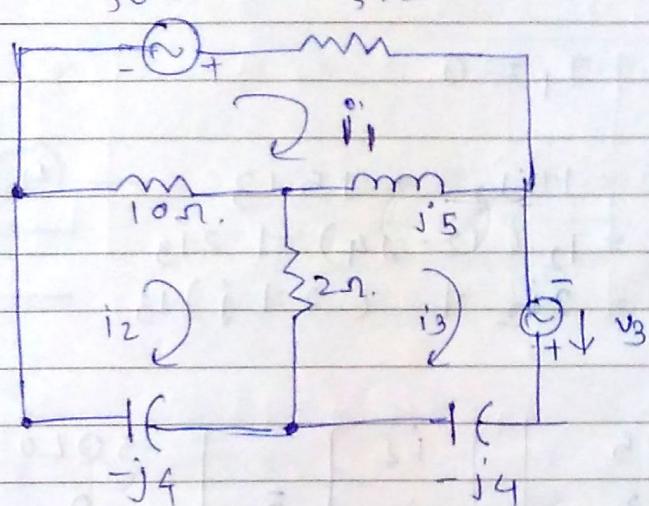

when $i_1 = 0$,
 $v_3 = ?$

$$\rightarrow 50 \angle 0^\circ - 5i_1 + j_5(i_3 - i_1) + 10(i_2 - i_1) = 0$$

$$\therefore 50 \angle 0^\circ + -15i_1 + j_5i_3 - j_5i_1 + 10i_2 = 0$$

$$\therefore 50 \angle 0^\circ = 15i_1 - 10i_2 + j_5i_3 - j_5i_3$$

$$\therefore 50 \angle 0^\circ = (15 + j_5)i_1 - 10i_2 - j_5i_3 \quad \text{--- (1)}$$

$$\rightarrow 10(i_1 - i_2) + 2(i_3 - i_2) + j_4i_2 = 0$$

$$\therefore 10i_1 - 12i_2 + 2i_3 + j_4i_2 = 0$$

$$\therefore 10i_1 - j_2(12 + j_4) + 2i_3 = 0 \quad \text{--- (2)}$$

~~10i1~~

• 9°. A.

$$\rightarrow 2(i_2 - i_3) + j_5(i_1 - i_3) + v_3 + j_4 i_3 = 0$$

$$\therefore v_3 = -2i_2 + 2i_3 - j_5 i_1 + j_5 i_3 - j_4 i_3$$

$$\therefore v_3 = -2i_2 + (2+j)i_3 - j_5 i_1 - j_4 i_3$$

Now, for $i_1 = 0$

$$50 \angle 0^\circ = -10i_2 - j_5 i_3 \quad (4)$$

$$0 = -j_2(12 - j_4) + 2i_3 \quad (5)$$

$$v_3 = -2i_2 + (2+j)i_3 \quad (6)$$

$$\begin{bmatrix} -10 & -j_5 \\ -(12 - j_4) & 2 \end{bmatrix} \begin{bmatrix} i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 50 \angle 0^\circ \\ 0 \end{bmatrix}$$

$$\therefore i_2 = \frac{\begin{vmatrix} 50 \angle 0^\circ & -j_5 \\ 0 & 2 \end{vmatrix}}{\begin{vmatrix} -10 & -j_5 \\ j_4 - 12 & 2 \end{vmatrix}}$$

$$\therefore i_2 = \frac{100}{-20 + j_5(j_4 - 12)}$$

$$= \frac{100}{-20 + 20j - j_5(12)}$$

$$= \frac{100}{-20 + 20j - 60j}$$

$$\therefore i_2 = \frac{100}{-20 - 40j} = 2.236 \angle 116.56^\circ$$

$$\text{and } i_3 = \begin{vmatrix} -10 & 50\angle 0^\circ \\ j_4 - 12 & 0 \end{vmatrix} \div -20 - 40j$$


$$= - \frac{50(j_4 - 12)}{-20 - 40j}$$

$$= \frac{-200j + 600}{-20 - 40j}$$

=

$$\rightarrow V_3 = 16.30V \angle 11.63^\circ$$

\Rightarrow Coupled circuits -

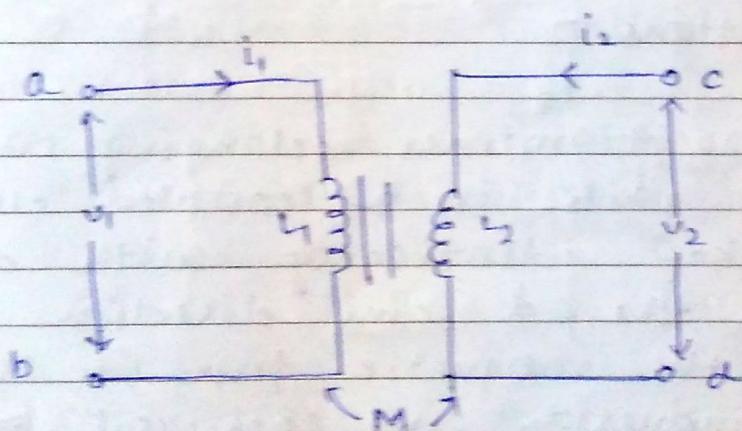


\rightarrow Two circuits are said to be coupled when energy transfer takes place from one circuit to another circuit by mutual induction.

self induced
voltage

Mutually induced
voltage

$$\text{so, } V_1 = L_1 \cdot \frac{di_1}{dt} + M \cdot \frac{di_2}{dt}$$
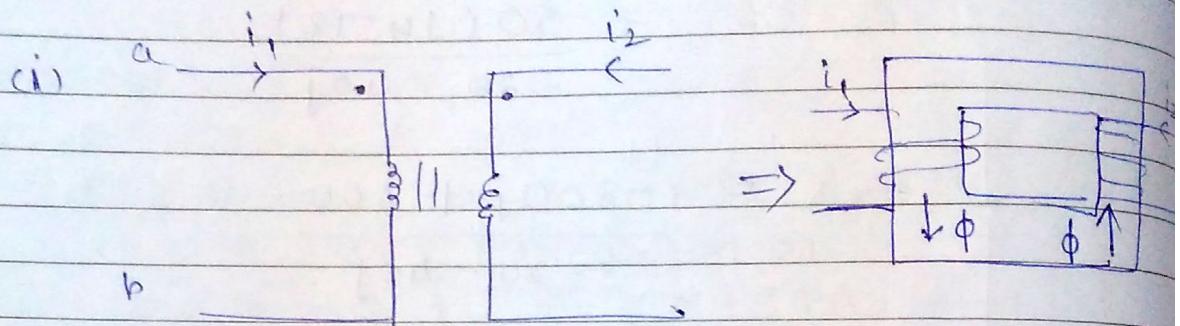
$$V_2 = L_2 \cdot \frac{di_2}{dt} + M \cdot \frac{di_1}{dt}$$



$$\text{so, } V_1 = L_1 \cdot \frac{di_1}{dt} + M \cdot \frac{di_2}{dt}$$

otherwise (negative).

⇒ Dot conventions -

(i) If the two terminals belonging to different coils in a coupled circuit are marked identically with dots then for the same direction of current, the magnetic flux of self and mutual induction in each coil ~~will be~~ together.

(ii) → If the current in one winding enters the dot mark and the current in other winding leaves the dot mark the voltages due to self and mutual

induction in any coil have opposite sign

(iii) If two coils are connected in series then,

$$L_{eq} = L_1 + L_2 \pm 2M.$$

\Rightarrow Energy stored in a coupled circuit -

$$(i) E = \frac{1}{2} LI^2 \text{ (for one coil).}$$

$$(ii) E = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 \pm M I_1 I_2$$

(for coils connected in series)

\Rightarrow Co-efficient of coupling -

It is defined as ~~diff~~ the fraction of total flux ~~linking~~ linking in coil denoted by K ,

$$K = \frac{\phi_{12}}{\phi_1} = \frac{\phi_{21}}{\phi_2} \quad (\phi_{12} = \text{flux linking in coil 1 due to coil 2})$$

$$\therefore \phi_{12} = \phi_{21} = K\phi_1 = K\phi_2$$

$$\therefore L_1 = \frac{N_1 \phi_1}{I_1}, \quad L_2 = \frac{N_2 \phi_2}{I_2}$$

$$M_{12} = \frac{N_1 \phi_{12}}{I_2}$$

$$M_{21} = \frac{N_2 \phi_{21}}{I_1}$$


$$\therefore M_{12} \times M_{21} = \frac{N_1 N_2 \cdot \phi_{12} \cdot \phi_{21}}{I_1 I_2}$$

$$= \frac{k^2 N_1 N_2 \phi_1 \phi_2}{I_1 I_2}$$

$$\therefore M^2 = L_1 L_2 k^2$$

$$\therefore k = \frac{M}{\sqrt{L_1 L_2}}$$

Ques.

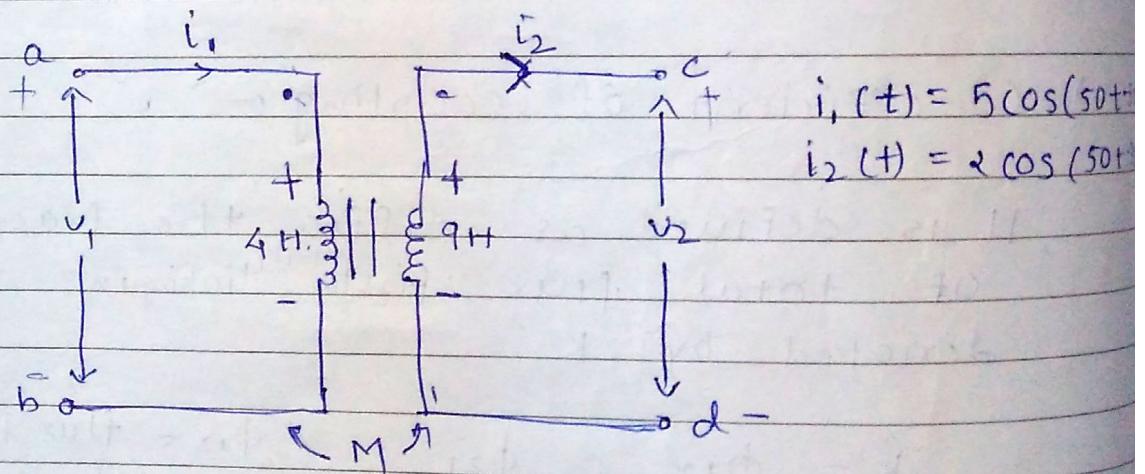

$$k = 0.5$$

find v_1 , v_2 and total energy stored at $t = 0$.

(Here i_1 is entering in dotted terminal & v_2 has positive reference at undotted terminal so, v_2 is negative. i_2 has positive undotted terminal)

$$v_1 = L_1 \cdot \frac{dI_1}{dt} + M \cdot \frac{dI_2}{dt}$$

$$\text{but } M = k \sqrt{L_1 L_2} \\ = 0.5 \sqrt{4 \times 9}$$

$$\therefore M = 3 \text{ H.}$$

$$\text{and, } \frac{di_1}{dt} = -5 \sin(50t - 30) \cdot 50$$

$$\therefore \frac{di_1}{dt} = -250 \sin(50t - 30)$$

$$\text{and } \frac{di_2}{dt} = -2 \sin(50t - 30) \cdot 50 \\ = -100 \sin(50t - 30)$$

~~$$\text{so, } v_1 = 5 \cos(50t - 30) \cdot [-250 \cdot \sin(50t - 30)] \\ + 3 \cdot [-100 \sin(50t - 30)].$$~~

~~$$= -1250 \sin(50t - 30) \cos(50t - 30) \\ - 300 \sin(50t - 30)$$~~

~~$$= -625 [\sin(100t - 60) + \sin(0)] \\ - 300 \sin(50t - 30)$$~~

~~$$\therefore v_1 = -625 \sin(100t - 60) - 300 \sin(50t - 30) \\ - 625 V. \\ = -625(-\sin 60) - 300(-\sin 30) - 625 \\ = 541.26 + 150 - 625$$~~

$$\text{and } V_2 = I_2 \cdot \frac{dI_2}{dt} - M \cdot \frac{dI_1}{dt}$$

$$= 2 \cos(50t - 30^\circ) \cdot [-100 \sin(50t - 30^\circ)] \\ - 3 (-250 \sin(50t - 30^\circ))$$

$$= 1.73(50) + 3(-125)$$

$$= 9 \cdot [-100 \sin(50t - 30^\circ)]$$

$$- 3 (-250 \sin(50t - 30^\circ))$$


$$= 450 - 375$$

$$\therefore V_2 = 75 \text{ V.}$$


$$\rightarrow \text{and } V_1 = 4 [-250 \sin(50t - 30^\circ)]$$

Network theorems.


⇒ Thvenin's theorem -

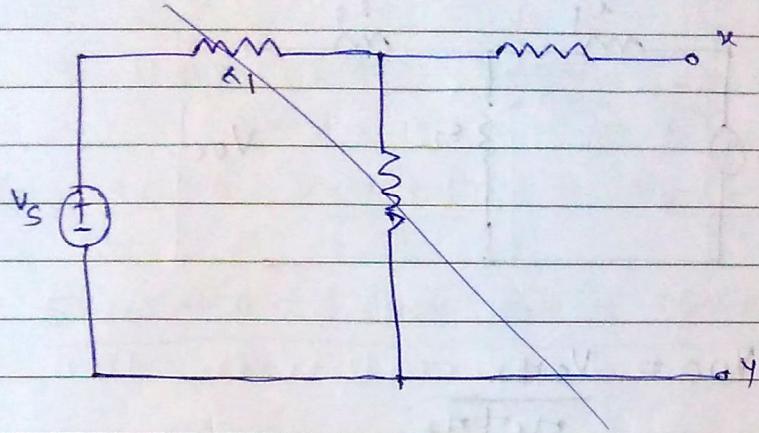

→ Any linear Active Network consisting of independent and/or dependent sources and linear bilateral Network elements can be replaced by an equivalent circuit consisting of a voltage source in series with a resistance. The voltage source be the open circuit voltage across the open circuited load terminals and the resistance be equivalent resistance of the network looking through the open circuited load terminals.

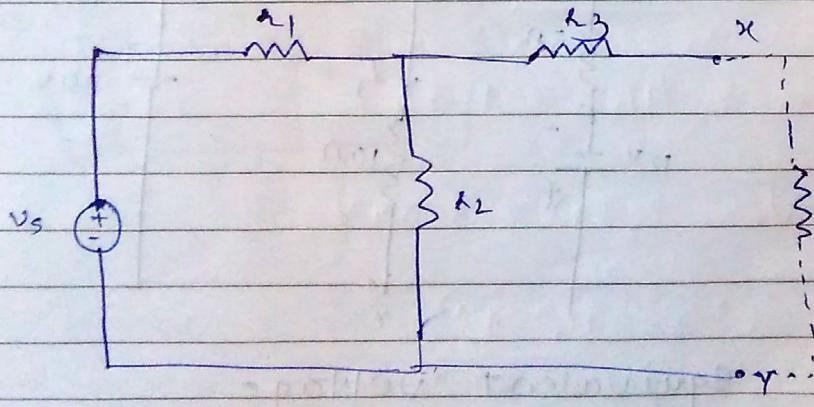


Remove Load,

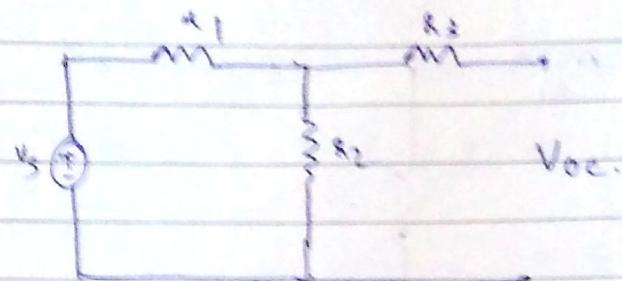


$$V_{oc} = \frac{V_s R_2}{R_1 + R_2}$$
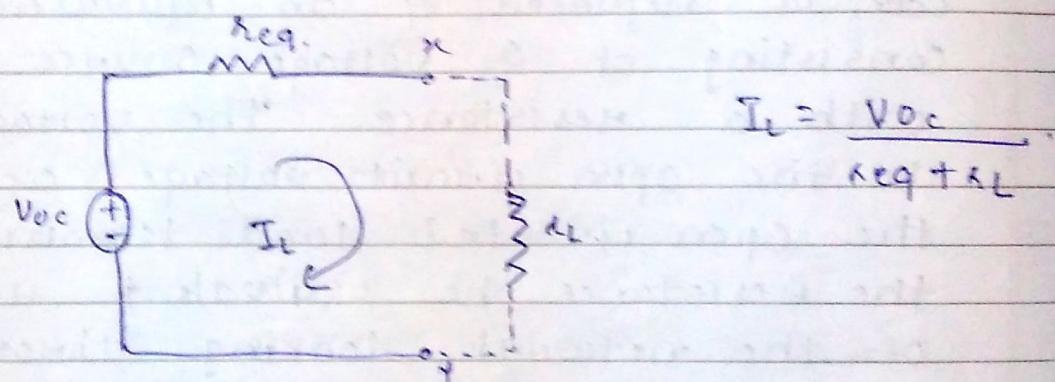
$$r_{eq} = \frac{R_1 R_2 + R_3}{R_1 + R_2}$$



Ques.

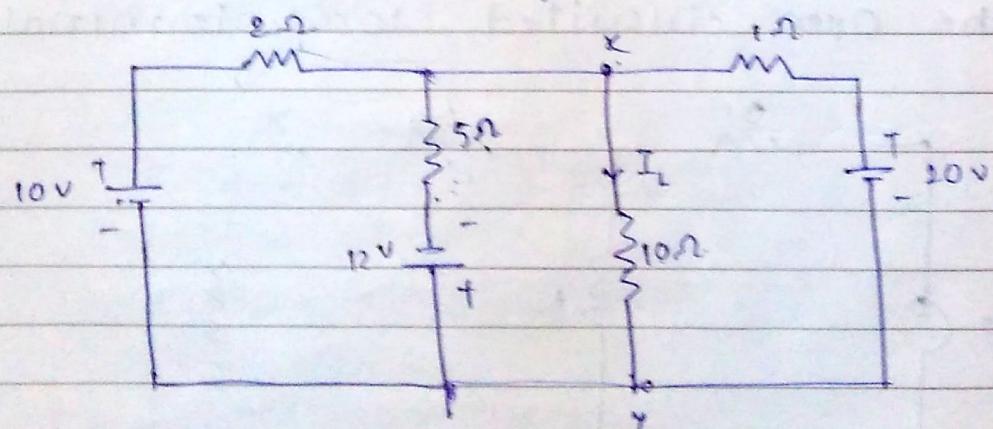

Here equivalent voltage.

We will remove 10Ω Resistor.

50. Open circuit voltage.

$$V_{xy} = 12 + \frac{10 \times 5}{7} = 19.14 \text{ V.}$$

$$\frac{V_{xy} - 10}{2} + \frac{V_{xy} + 12}{5} + \frac{V_{xy} - 20}{1} = 0$$


$$\therefore \frac{5V_{xy} - 50}{10} + \frac{2V_{xy} + 24}{10} + \frac{10V_{xy} - 200}{10} = 0$$

$$17V_{xy} - 226 = 0$$


$$\therefore V_{xy} = 13.29 \text{ V.}$$

$$\rightarrow R_{eq} = \frac{\left(\frac{5 \times 2}{7}\right)(1)}{\frac{5 \times 2}{7} + 1}$$
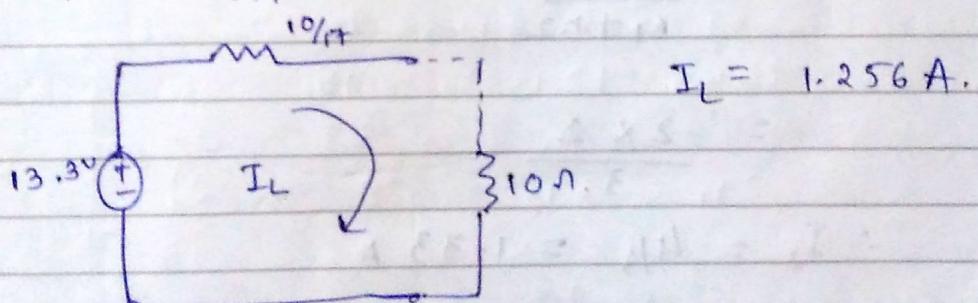
$$\therefore R_{eq.} = \frac{10}{17} \Omega$$



$$I_L = 1.256 \text{ A.}$$

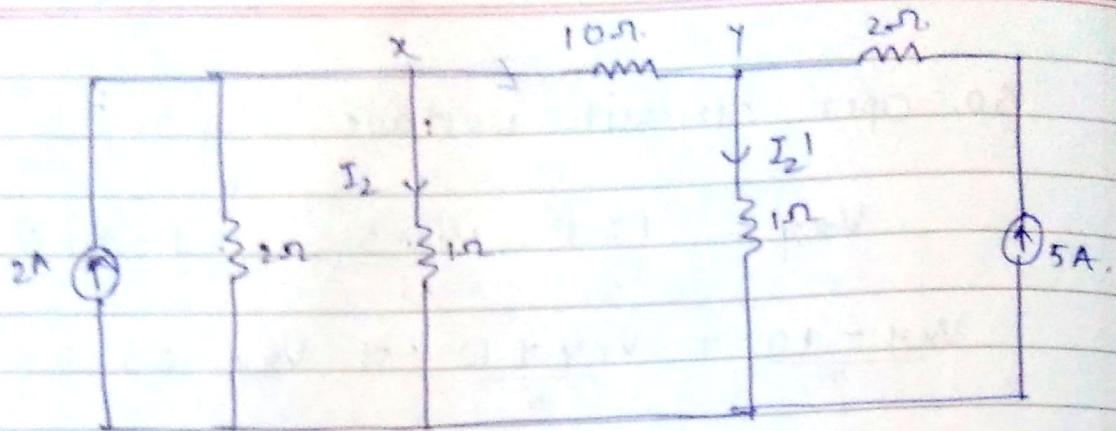Ques.

Now find power loss in 10Ω Register

→ Now, we will find open circuit ~~voltage~~ ^{voltage}.

$$R_{eq} = \frac{2 \times 1}{3}$$

$$V_{xy} = V_x - V_y$$

by using current division rule,

$$I_2 = \frac{\kappa_1 I}{\kappa_1 + \kappa_2}$$

$$= \frac{2 \times 2}{3}$$

$$\therefore I_2 = \frac{4}{3} = 1.33 \text{ A}$$

$$\therefore V_x = I_2 (1) = 1.33 \text{ V}$$

~~$$\rightarrow \text{And. } I_2' = \frac{\kappa_1' I'}{\kappa_1' + \kappa_2'}$$~~

~~$$\therefore I_2' = \frac{2 \times 5}{3} = 10/3$$~~

~~$$\therefore V_y = I_2' (1) = 5 \text{ V}$$~~

$$\therefore V_{xy} = V_x - V_y$$


$$\therefore V_{xy} = -3.67 \text{ V}$$

→ Here, we have to remove current source.

so, 2 and 1 Ω will be in parallel and another 3Ω will be in series.


$$\begin{aligned} R_{eq} &= \frac{1 \times 2}{3} + 1 \\ &= 2\frac{1}{3} + 1 \end{aligned}$$
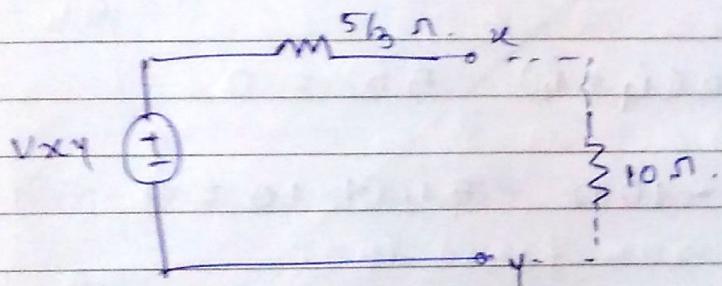
$$\therefore R_{eq} = 5\frac{1}{3} \Omega.$$



$$I_L = \frac{-3.67}{11.66} = 0.3195 \text{ A.}$$

$$\text{and } P_{10} = 0.99 \text{ Watts.}$$

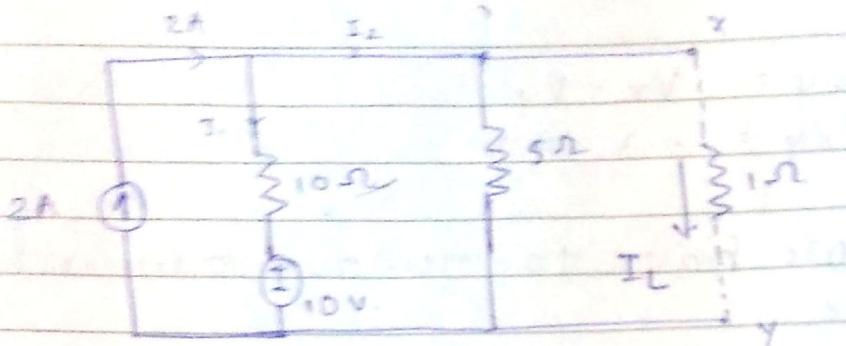Ques.

→ Here we will find an open circuit voltage, V_{xy} .

Here, for first loop, KVL:

$$10 + 10i_1 = 2 \rightarrow ① \quad 2 + 10(i_2 - i_1) - 10 = 0 \\ \therefore -10i_1 + 10i_2 - 8 = 0$$

and for second loop, KVL: $10i_1 - 10i_2 = -8$
 $\therefore 5i_1 - 5i_2 = -4 \quad ②$

$$10 + 10(i_2 - i_1) - 5i_2 = 0.$$

$$\therefore 10i_1 - 10i_2 - 5i_2 + 10 = 0$$

$$\therefore 10i_1 - 15i_2 = -10$$

$$\therefore 2i_1 - 3i_2 = -2 \quad ③$$


$$\left| \begin{array}{l} i_1 = 2 \\ i_2 = 2A \\ V_{xy} = 10V \end{array} \right.$$

$$\frac{V_{xy} - 10}{10} + \frac{V_{xy}}{5} = 2$$

$$\therefore V_{xy} = 10V.$$

$$\text{and } R_{eq} = 10 \parallel 5$$

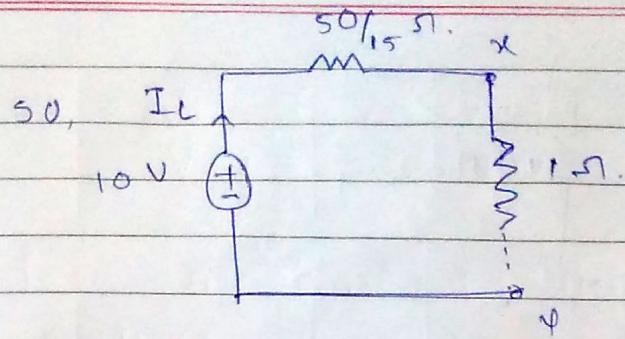
$$\therefore R_{eq} = \frac{50}{15} \Omega.$$



$$10 - I_L (\frac{50}{15} + 1) = 0$$

$$\therefore I_L = \frac{10}{\frac{50}{15} + 1} = 2.30 \text{ A.}$$

Ques

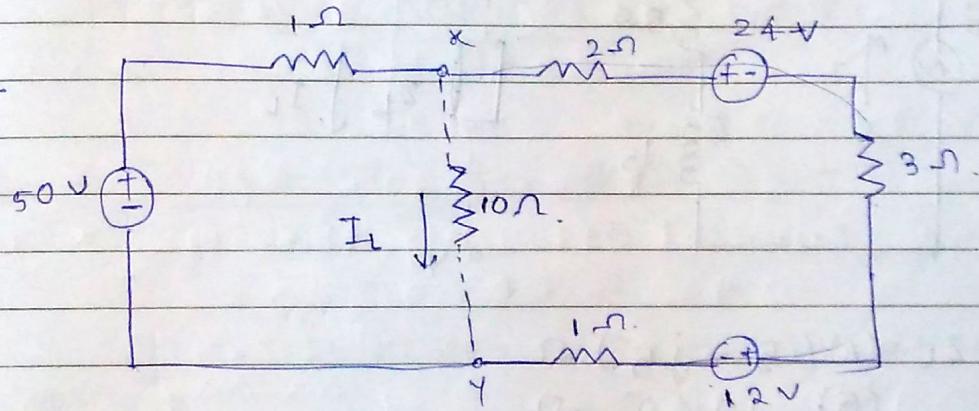

Here, Open circuit voltage,

$$\frac{V_{xy} - 50}{1} + \frac{V_{xy} - 24 - 12}{6} = 0$$

$$\therefore 6(V_{xy} - 50) + V_{xy} - 36 = 0$$


$$\therefore 7V_{xy} - 300 - 36 = 0$$

$$\therefore V_{xy} = 48 \text{ V.}$$


$$\text{and } R_{eq} = \cancel{2 + 3 + 1} \parallel 1$$

$$\therefore R_{eq} = \frac{1}{4} \Omega.$$

;

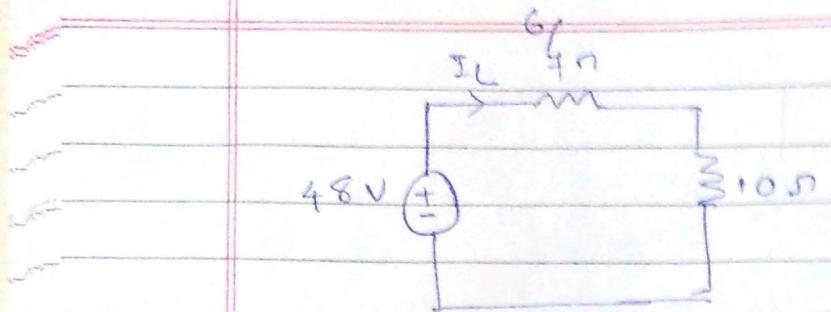
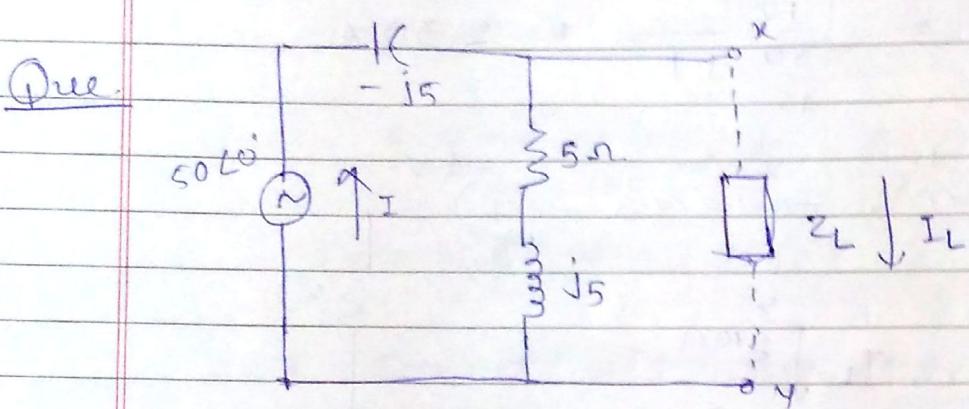
$$\therefore I_L = \frac{48}{6 + 10} = 4.42 \text{ A.}$$



$$Z_L = (A)(5 - j5) \Omega$$

$$(B) 10 \angle 0^\circ \Omega$$

Here, KVL for first loop,

$$50 - (-j5)I - 5I - j5(I) = 0$$

$$\therefore 50 + I(j5) - 5I - j5(I) = 0$$


$$\therefore 50 = 5I$$

$$\therefore I = 10 \text{ A.}$$

$$\therefore V_{xy} = 5(10) + j5(10)$$

$$\therefore V_{xy} = 50 + 50j$$

and,

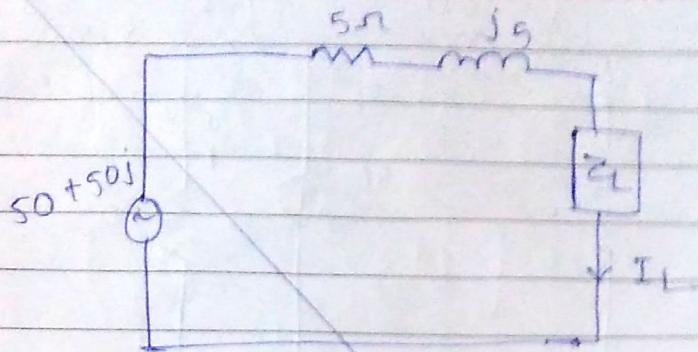

$$\checkmark \quad I = \frac{50 + 50j}{5 + j5 + 5 - j5}$$

$$\therefore I_L = \frac{50 + 50j}{10} = 5 + 5j = 7.07 \angle 45^\circ$$

OR

$$\frac{V_{xy} - 50}{-j5} + \frac{V_{xy} - 0}{5 + j5} = 0 \quad (\text{By node analysis})$$

$$\therefore (5 + j5)(V_{xy} - 50) + V_{xy}(-j5) = 0$$

$$\therefore 5V_{xy} - 250 + V_{xy}(-j5) - 50j5 \\ \cancel{+ -V_{xy}(j5)} = 0$$

$$\therefore V_{xy} - 50 - 10j5 = 0$$


$$\therefore V_{xy} = 50 + 50j.$$

and, for $Z = 10 \angle 0^\circ$.


$$I_L = \frac{50 + 50j}{5 + j5 + 10} = \frac{50 + 50j}{15 + 5j}$$

$$\therefore I_L = (2 + j4) A$$

Q. 11.

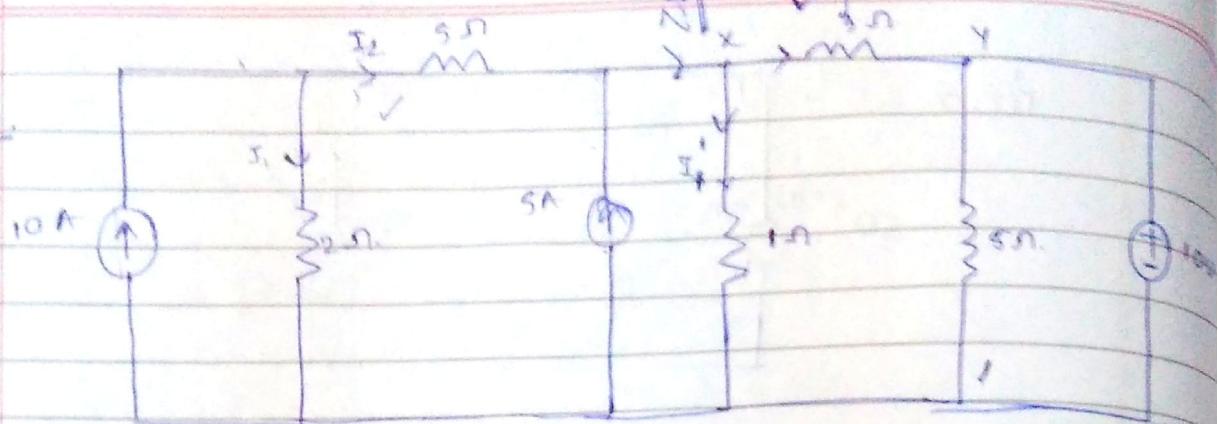

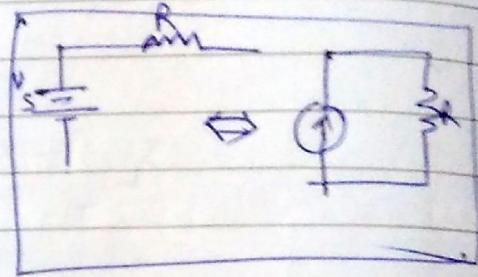
$$\begin{aligned} I_2 &= \frac{R_1 I}{R_1 + R_2} \\ &= \frac{2 \times 10}{2 + 9} \\ &\Rightarrow I_2 = 2.85 \text{ A.} \end{aligned}$$



so, current flowing through a node
 $= 2 + 5 = 7 \text{ A.}$

$$\begin{aligned} I_1' &= \frac{R_2 I}{R_1 + R_2} \\ &= \frac{3 \times 7}{4} \\ &\Rightarrow I_1' = 5.25 \text{ A.} \end{aligned}$$

$$V_x = 5.25 \text{ V.}$$

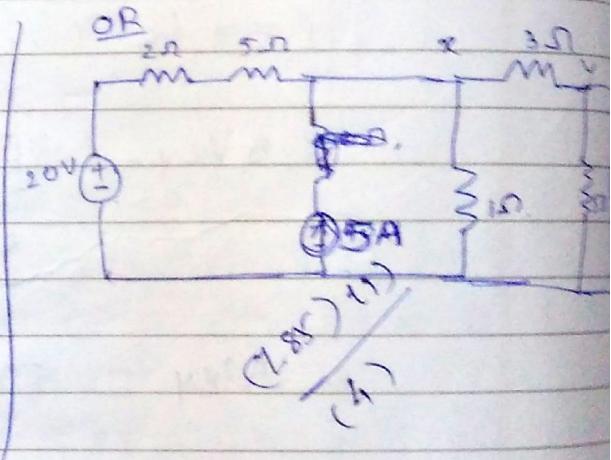

and $V_y = 10 \text{ V.}$

- 5

$$\text{Note, } \frac{V_x - 20}{7} + \cancel{\frac{V_x - 10}{2}} + V_x = 0$$


$$\therefore 2V_x - 40 + 7V_x - 70 + 14V_x = 0$$

$$\therefore 23V_x = 110 \quad \therefore V_x = 6.875$$

$$\therefore V_{xy} = -3.125 \text{ V}$$

$$\text{and } R_{eq} = 7\Omega + 5 \Omega = \frac{7+5}{8} \Omega$$
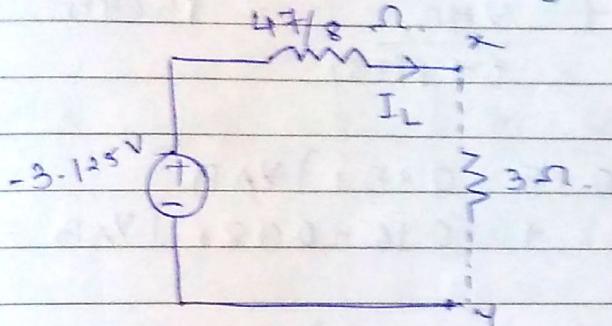
$$\therefore R_{eq} = 4\frac{7}{8} \Omega$$




$$\text{so, } I_L = \frac{-3.125}{4\frac{7}{8} + 3} = \frac{-3.125}{8.875}$$

$$\therefore I_L = -0.352 \text{ A}$$

$I = 15 \text{ A} 45^\circ$

Ques.

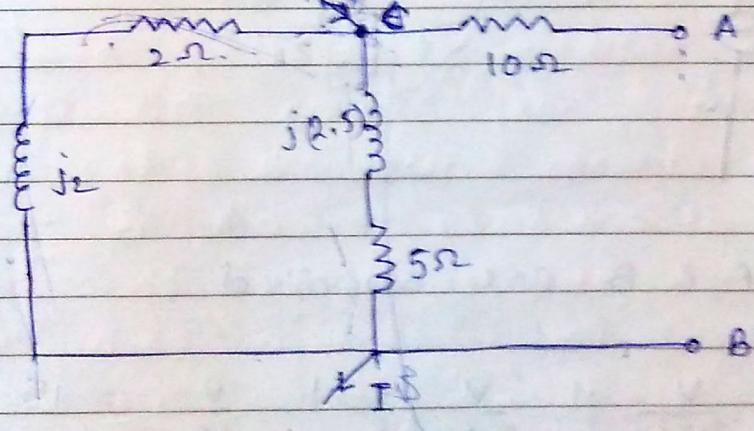

find our
current if
A & B are
shorted.

→ Here, first we will find open circuit voltage,

$$\text{so, } \frac{V_{AB}}{12+2j} + \frac{V_{AB}}{15+2.5j} = 0.$$

$$\therefore V_{AB} \left[\frac{1}{12+2j} + \frac{1}{15+2j} \right] = 0.$$


$$\text{so, } \frac{V_{AB}}{2+2j} + \frac{V_{AB}}{5+j(2.5)} = 15 \angle 45^\circ$$

$$\therefore \cancel{V_{AB}} (0.25 - 0.25j) V_{AB} + (0.16 - 0.08j) V_{AB} = 15 \angle 45^\circ$$

$$\therefore (0.41 \cancel{- 0.33j}) V_{AB} = 10.68 + 10j$$

$$\therefore V_{AB} = 28.50 \angle 83.82^\circ$$


Req.

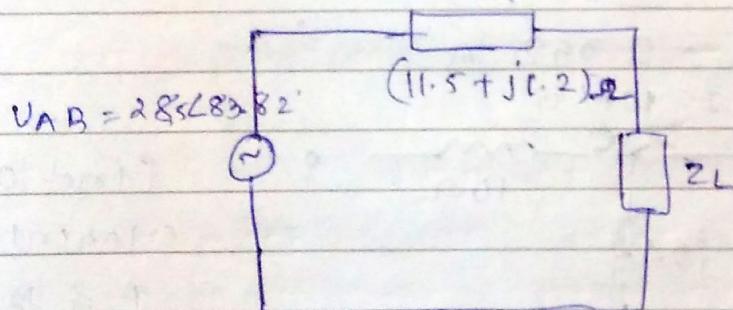

→ Now, A & B are shorted.

$$\text{so, } \frac{V}{2+j2} + \frac{V}{5+j2.5} + \frac{V}{10} = 15 \angle 45^\circ$$

$$\therefore V = 24.7 \angle 77^\circ V$$

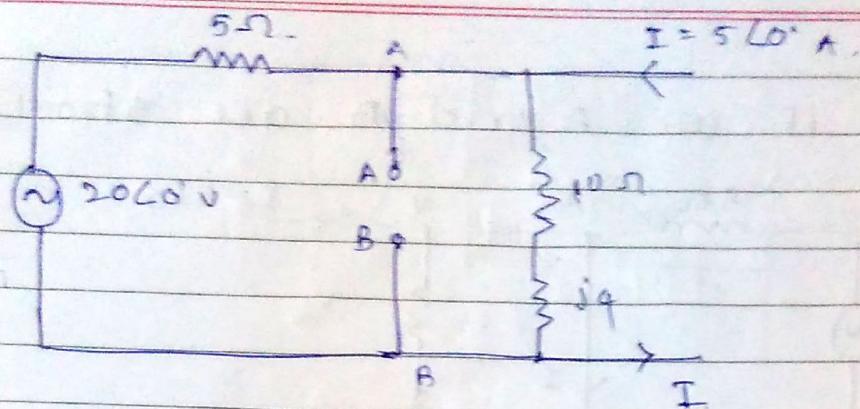Ques

→ Here,

$$\frac{V_{AB} - 20}{5} + \frac{V_{AB}}{10 + 4j} = 5\angle 0^\circ$$

$$\therefore V_{AB} - 20(10 + 4j) + 5V_{AB} = 5(5)(10 + 4j)$$

$$\begin{aligned} \therefore 10V_{AB} + 4V_{AB}j - 200 - 80j + 5V_{AB} \\ = 250 + 100j \end{aligned}$$

$$\therefore 15V_{AB} + 4V_{AB}j = 450 + 180j$$

$$\therefore V_{AB} [15 + 4j] = 450 + 180j$$


$$\therefore V_{AB} = 31.22 \angle 6.86^\circ$$

$$\begin{aligned} \rightarrow Z_{eq} &= 5 \parallel (10 + 4j) \\ &= \frac{5(10 + 4j)}{5 + 10 + 4j} \end{aligned}$$

$$= \frac{50 + 20j}{15 + 4j}$$

$$\therefore Z_{eq} = 3.46 \angle 6.87^\circ$$

→ Now, if A and B are short-circuited.

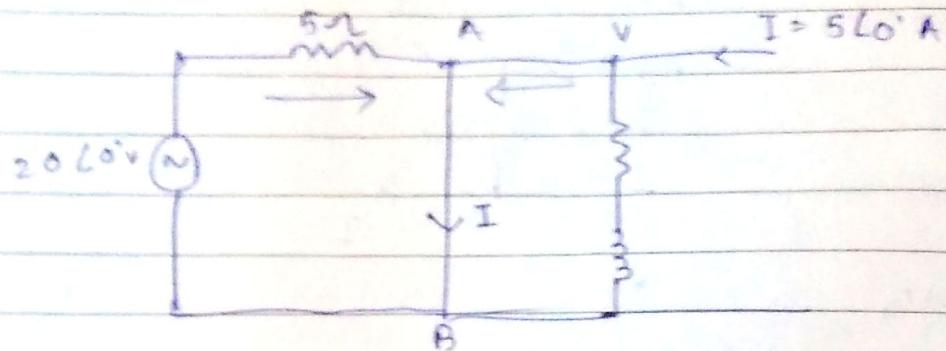


$$\frac{V_{AB} - 20}{5} = 5$$

$$\therefore V_{AB} - 20$$

$$\text{Hence, } \frac{20}{5} = 4 \text{ A.} + 5 \text{ A.} = 9 \text{ A.}$$


⇒ Superposition theorem -

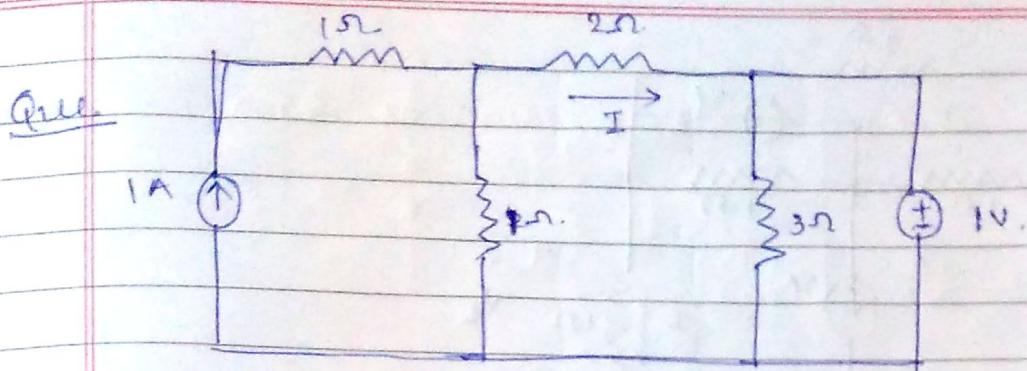Statement: If a number of voltage and current sources are acting simultaneously in a linear network, the resultant current in any branch is the Algebraic sum of the currents that would be produced in it when each source acts alone. Replacing all other voltage sources by short-circuit and current sources by open-circuit.



$$I_2 = ?$$

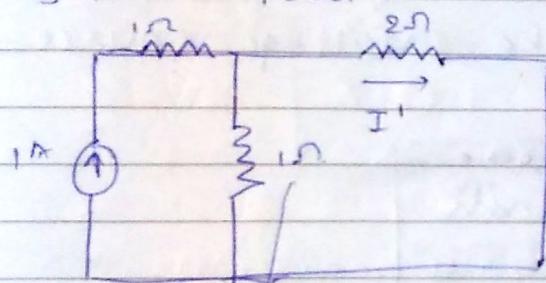
→ Here, we will make voltage source as short circuit



$$I' = \frac{I(1)}{1+2} = I_{1g}$$

$$\therefore I' = \frac{1}{3} A.$$

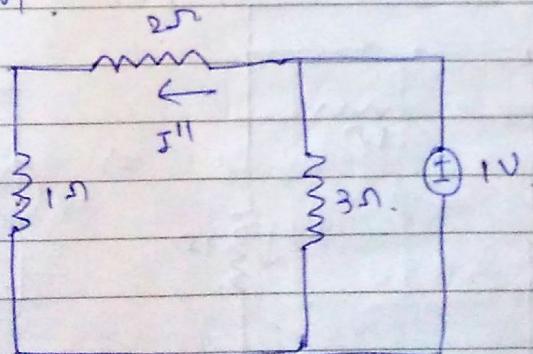
→ Now, we will make current source as open.




$$\text{Here, } I'' = \frac{V}{1+2} = \frac{1}{3} = \frac{1}{3} A.$$

$$\text{So, Resultant current } I = I' - I'' = \frac{1}{3} - \frac{1}{3} = 0 A.$$


Ques.

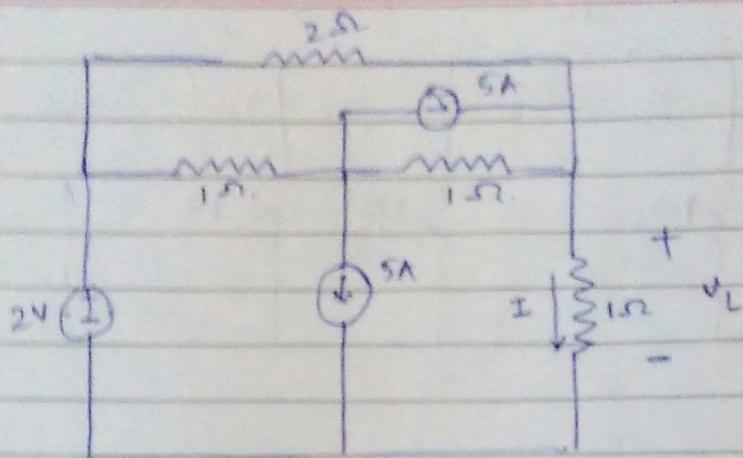find out V_L Using Super-position theorem

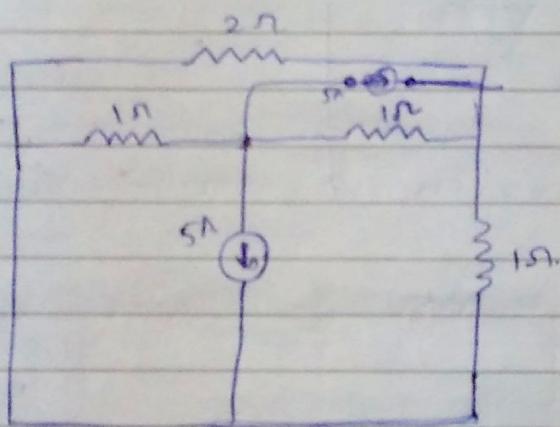→ Now we will make voltage source as short.




→ making current source as open

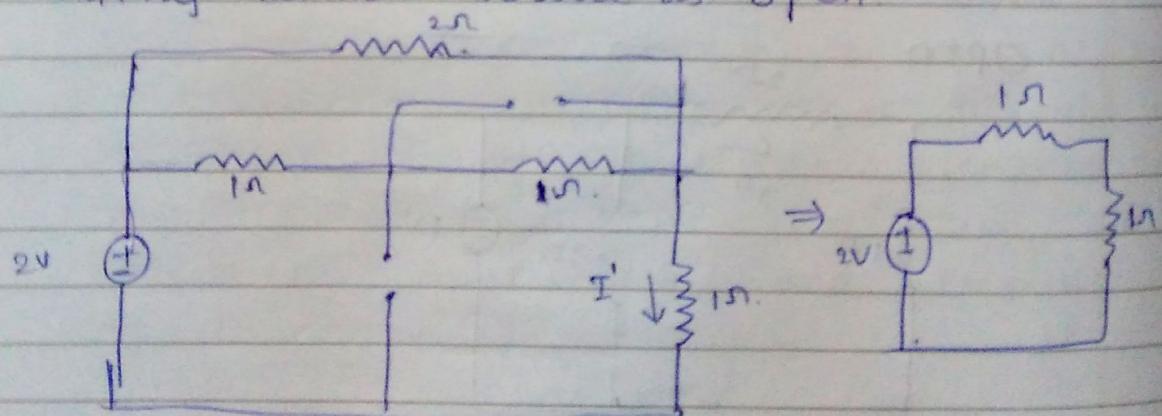

$$\text{so, } I' = \frac{2}{2} = 1 \text{ A}$$

$$\therefore V_L = 1 \text{ V.}$$

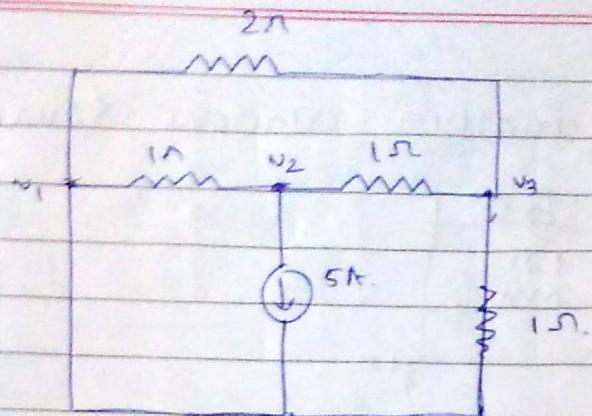

~~$\frac{v_1 - v_3}{2} + 2\left(\frac{v_1 - v_2}{2}\right) = 0$~~

~~$v_1 - v_3 + 2v_1 - 2v_2 = 0$~~

~~$\therefore 3v_1 - 2v_2 - v_3 = 0 \quad \text{--- (1)}$~~

~~$\frac{v_2 - v_1}{1} + \frac{v_2 - v_3}{1} + \frac{5}{1} = 0$~~

~~$2v_2 - v_1 - v_3 + 5 = 0$~~

~~$\therefore v_1 - 2v_2 + v_3 = 5 \quad \text{--- (2)}$~~

~~$\frac{v_3 - v_1}{2} + 2\left(\frac{v_3 - v_2}{2}\right) + 2\frac{v_3}{2} = 0$~~

~~$v_3 - v_1 + 2v_3 - 2v_2 + 2v_3 = 0$~~

~~$\therefore 5v_3 - v_1 - 2v_2 = 0$~~

~~$\therefore v_1 + 2v_2 - 5v_3 = 0 \quad \text{--- (3)}$~~

~~$v_3 = -5$~~

Here, $v_1 = 0$,

~~$v_3 = I''$~~

~~$-2v_2 + v_3 = 5 \text{ and}$~~

~~$2v_2 - 5v_3 = 0$~~


~~$\therefore I'' = v_3$~~

~~$\therefore I'' = -5A$~~



$$-4v_3 = 5$$

$$\boxed{\therefore v_3 = -5/4 V}$$

Now taking another current source.

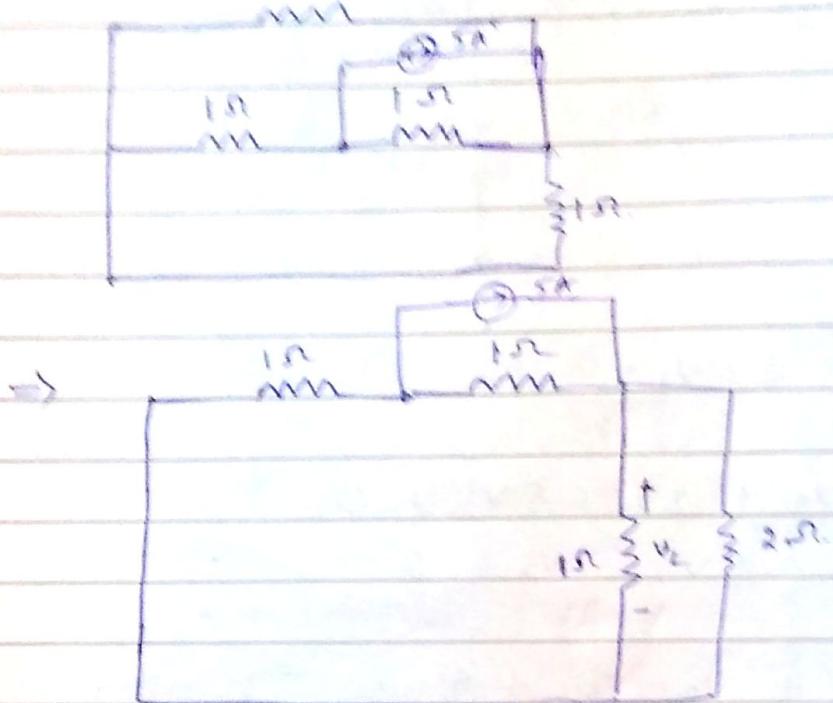

Using Source-transformation.

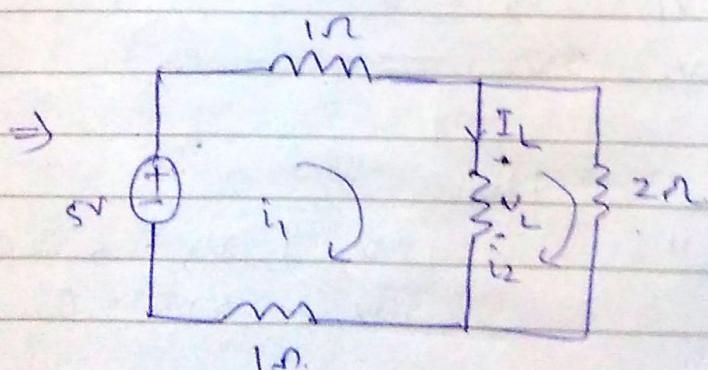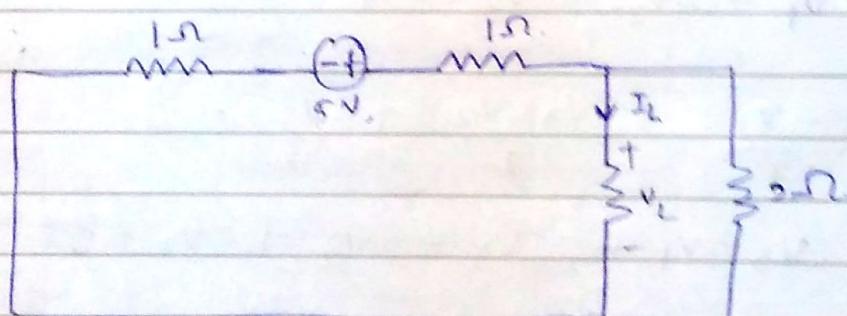

for loop - 1,

$$5 - i_1 + v_L - i_L = 0$$
$$\therefore 5 - 2i_1 = v_L \quad \text{---(1)}$$

-> fun loop - 2,

$$V_L = 2i_2 = 0$$

$$\therefore V_L = 2i_2 \rightarrow (2)$$

$$\text{so, } 5 - 2i_1 = 2i_2$$

$$\therefore 2i_1 + 2i_2 = 5 \rightarrow (3)$$

$$\text{and } V_L = (i_2 - i_1),$$

$$V_L = 1(i_1 - i_2) \rightarrow (4)$$

$$2i_2 = i_1 - i_2$$

$$(3i_2 = i_1)$$

$$5 - 2i_1 = i_1 - i_2$$

$$\therefore 5 - 3i_1 = -i_2$$

$$\therefore 5 - 9i_2 = -i_2$$


$$\therefore 5 - 2i_1 = i_2 - i_1$$

$$\therefore i_1 + i_2 = 5 \rightarrow (4)$$

$$\begin{aligned} & 5 - 8i_2 \\ & 2i_2 = 5 \\ & i_2 = \frac{5}{2} \end{aligned}$$



$$\begin{aligned} & 2i_2 = 5 \\ & i_2 = \frac{5}{2} \\ & \frac{15}{8} \\ & \frac{75}{8} \\ & \frac{75}{8} - \frac{48}{8} = \frac{27}{8} \end{aligned}$$

Ques.

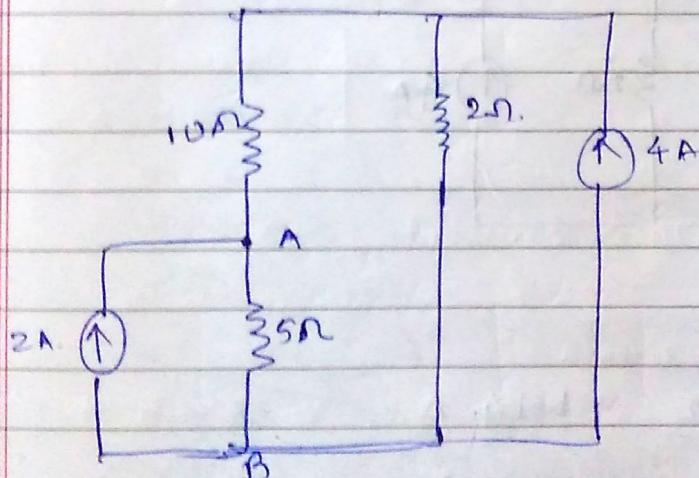

Find $V_{AB} = ?$

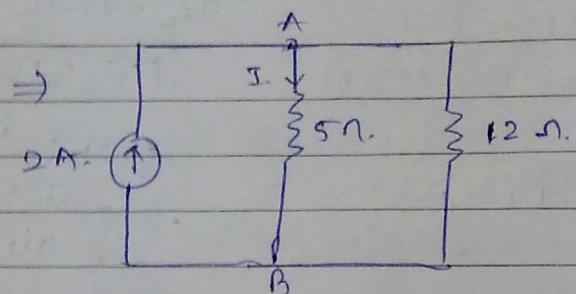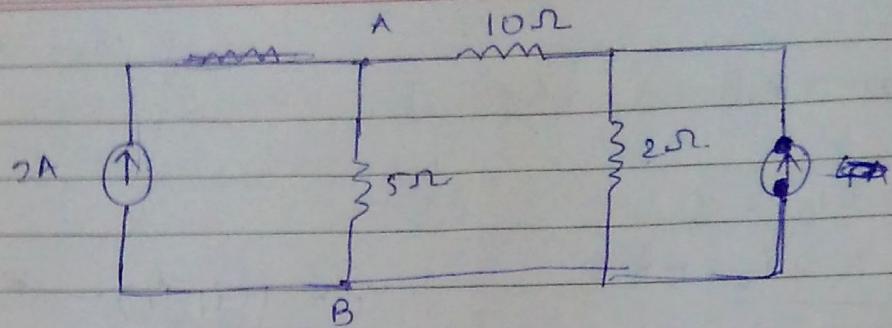
→ Making 4A current source as open circuit



$$I = \frac{2 \times 12}{17} = 1.41 \text{ A.}$$

$$\therefore V_{AB}^1 = \underline{7.05 \text{ V.}}$$

→ Now making 2A as Open circuit,

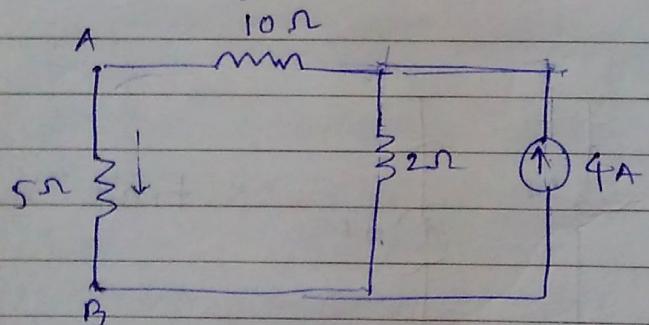

$$\text{So, } I' = \frac{4 \times 2}{17} = \cancel{1.4} \text{ A.}$$

$$\therefore V_{AB}'' = \underline{2.35 \text{ V}}$$

$$\text{So, } V_{AB} = V_{AB}^1 + V_{AB}''$$

$\therefore V_{AB} = \underline{\underline{9.4}}$

⇒ Maximum Power transfer theorem -

- It is used to find the value of Load resistance for which there would be max. power transfer from source to load.
- A Resistive load being connected to a DC network, receives max. power when the load resistance is equal to the equivalent resistance of the network as seen from the load terminals.

$$I_L = \frac{V_{oc}}{R_{eq} + R_L}$$

$$\therefore P_L = V_{oc} I_L^2 R_L$$

$$\therefore P_L = \left(\frac{V_{oc}}{R_{eq} + R_L} \right)^2 R_L \quad \text{--- (1)}$$

→ For Max. power,

$$\frac{dP_L}{dR_L} = 0$$

~~$$\therefore \left(\frac{V_{oc}}{R_{eq} + R_L} \right)^2 + R_L \cdot \frac{2V_{oc}}{R_{eq} + R_L}$$~~

~~$$\therefore (V_{oc})^2 \left[\frac{R_L}{(R_{eq} + R_L)^2} \right] =$$~~

~~$$\therefore V_{oc}^2 \left[\frac{R_L \cdot \frac{1}{R_{eq} + R_L}}{(R_{eq} + R_L)^2} \right]$$~~

$$= V_{oc}^2 \left[R_L \cdot \frac{1}{(R_{eq} + R_L)^2} + \frac{1}{R_{eq} + R_L} \right]$$

$$= \frac{V_{oc}^2}{R_L + R_{eq}} \left[\frac{-R_L}{R_{eq} + R_L} + 1 \right]$$

$$= \frac{V_{oc}^2}{R_L + R_{eq}} \left[\frac{R_{eq}}{R_{eq} + R_L} \right]$$


$$\Rightarrow V_{oc}^2 \left[\frac{R_{eq} L}{(R_{eq} + R_L)^2} \right] = 0$$

$$(R_{eq} + R_L)^2 (1) - 2(R_{eq} + R_L)(R_L) (1) = 0$$

$$\Rightarrow R_{eq}^2 + 2R_{eq}R_L + R_L^2 - 2R_{eq}R_L - 2R_{eq}R_L = 0 \\ \Rightarrow R_{eq}^2 = 0 \Rightarrow R_{eq} = 0$$

$$\therefore R_L = R_{eq}$$

$$P_{max} = \frac{V_{oc}^2}{4R_L}$$

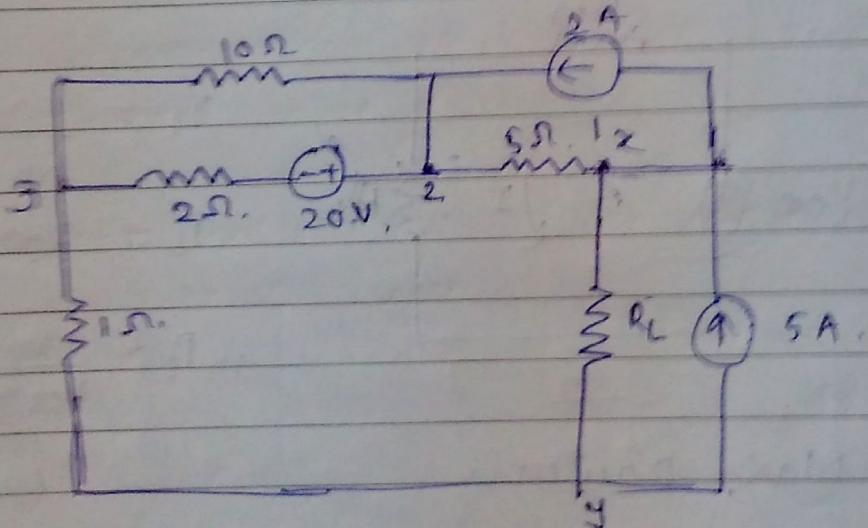

Here, xy is open circuit,

→ Using Nodal Analysis,

$$\frac{V_1 - V_2}{5} = 5 - 2$$

$$\therefore \frac{V_1 - V_2}{5} = 3$$

$$\therefore V_1 - V_2 = 15 \quad \text{--- (1)}$$

$$\frac{V_2 - V_4}{5} + \frac{V_2 - V_3}{10} = 5$$

for node - 3,

$$\frac{v_3 - v_2}{10} + \frac{v_3 + 20}{2} + \frac{v_3}{1} = 0$$

for node - 2,


$$\frac{v_2 - 20 - v_3}{2} + \frac{v_2 - v_1}{5} + \frac{v_2 - v_3}{10} = 2$$

$$\therefore 5\left(\frac{v_2 - 20 - v_3}{10}\right) + 2\left(\frac{v_2 - v_1}{5}\right) + \frac{v_2 - v_3}{10} = 2$$

$$5v_2 - 100 - 5v_3 + 2v_2 - 2v_1 + v_2 - v_3 = 20$$


$$\therefore -2v_1 + 8v_2 - 6v_3 = 120$$

$$\therefore -v_1 + 4v_2 - 3v_3 = 60$$

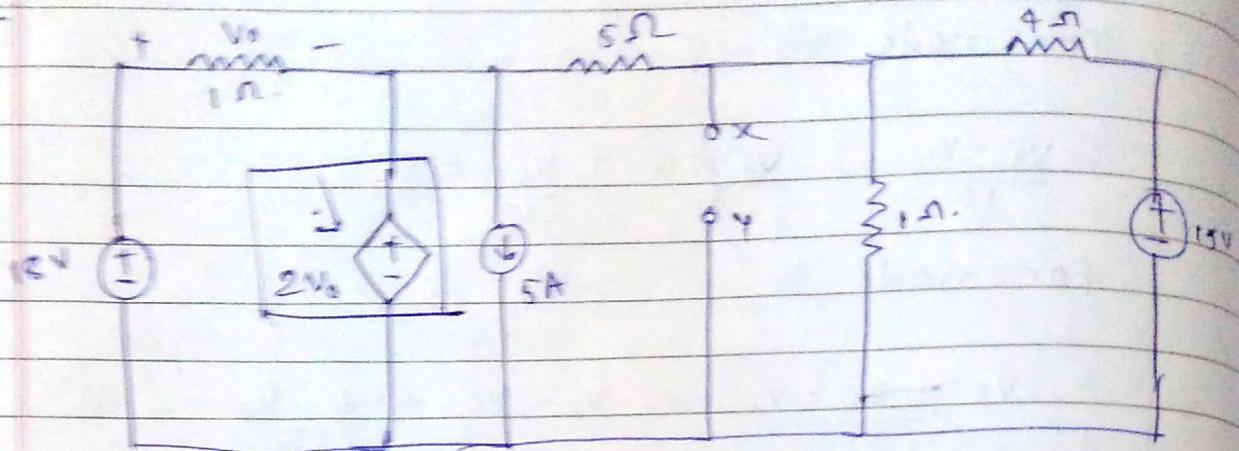
M.JafDate

Using Super-position theorem, find the Thevenin's equivalent circuit for the portion of the network at the left of terminals x-y. also find the current through 1Ω resistance at the right hand side of terminal x-y.

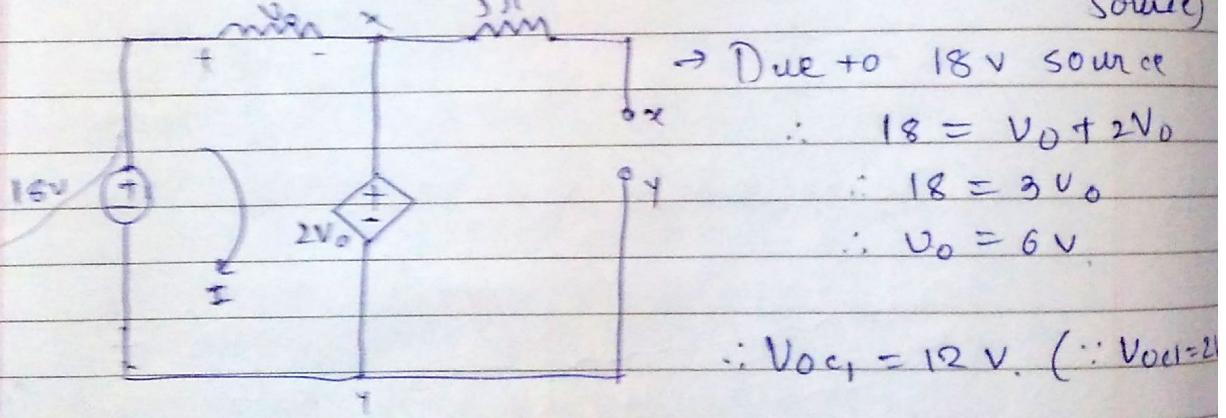→ For left network, (we can't remove dependent source)



→ Due to 5A source,

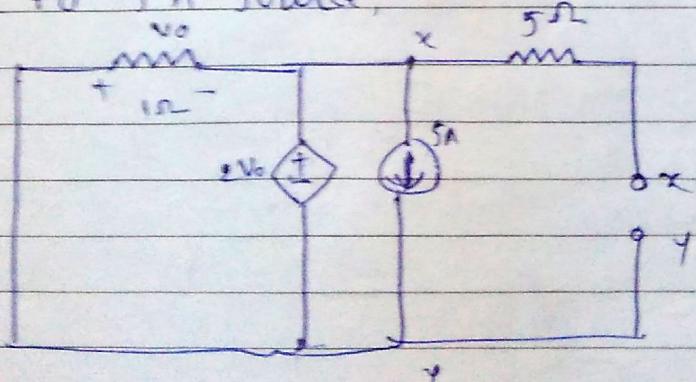


Vising Model

$$\frac{V_o}{1} + V_o = V_o$$

→ Mesh equation,

$$2V_o + V_o = 0$$

$$\therefore V_o = 0$$

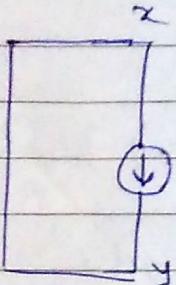

$$\text{so, } V_{oc\ 2} = 0.$$

$$\begin{aligned} \text{so, } V_{oc} &= V_{oc1} + V_{oc2} \\ &= 12 + 0 \end{aligned}$$

$$\therefore V_{oc} = 12V$$

→ ~~$I_{oc} = R_{eq} = 5\Omega$~~


$$\therefore \underline{\underline{I_{oc}}} =$$

Thevinin

→ Here Dependent source is present. So, we have to find I_{sc} first.

$$I_{sc} = \frac{V_{oc}}{5} = 12/5 \text{ A.}$$
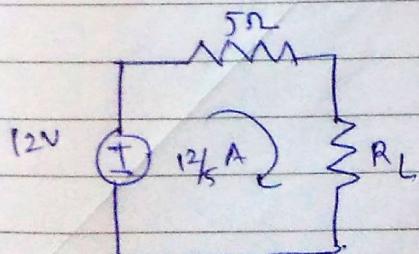
$$R_{eq} = \frac{V_{oc}}{I_{sc}} = \frac{12}{12/5} = 5\Omega$$



Thevinin's eq. circuit.

classmate

Date _____

Page _____